

Antenna Tuners (Antenna Couplers)

What is an Antenna Tuner?

- An antenna tuner (coupler is a more correct term) is an impedance matching device which minimizes “mismatch” loss (maximizes power transfer).
- NOT different from any other impedance matching circuit. It does NOT tune the antenna!
- Old R.L. Drake devices were named MN-4, MN-2000, MN-2700. Guess what the MN stands for.
- Also referred to as coupler, antenna coupler, transmatch, Matchbox, etc.

Basics: Correct or Incorrect?

- An antenna operated at its resonant frequency doesn't need a coupler.
 - *No, resonance only means the feed point is resistive and does not mean a low SWR.*
- Resonant antennas radiate better than non-resonant antennas.
 - *No, pattern may change from that at resonance and will need to match.*
- Most antennas are resonant at only one frequency.
 - *No, all antenna have multiple resonances.*

Basics: Correct or Incorrect?, Page 2

- The ability to match is more important than efficiency when choosing a coupler.
 - *Yes, if the coupler doesn't match not much else matters.*
- Coupler affects magnitude of current to antenna.
 - *Yes, this is how matching works.*
- Coupler does not affect the pattern of the antenna.
 - *Should be Yes, but only if the ratio of any common mode current on the feed line to the antenna currents remains the same.*

Basics: Correct or Incorrect?, Page 3

- The SWR presented by an antenna is minimum at the fundamental resonant frequency.
 - *No, often SWR is minimum but not a requirement.*
- A coupler placed at the antenna will always result in a more efficient system than one placed at the transmitter.
 - *Generally Yes, but impedance at antenna is different and coupler might not be able to match or be as efficient for this impedance.*

Basics: Correct or Incorrect?, Page 4

- Does 50 Ω coax need to be used between coupler and transmitter?
 - *No, but do not use SWR meter in coupler if not 50 Ω .*
- True open wire #12ga. 600 Ω transmission line has lower loss than 1/2" 50 Ω coax.
 - *Generally Yes, however if load is 5+j0, SWR on 50 Ω line is 10:1 & 120:1 on open wire line. Loss for 100' at 7MHz is 2.12dB (open wire) & 1.02dB (LMR-500).*
- Couplers should not be cascaded.
 - *Yes, if both auto-couplers but no otherwise.*

Basics: Correct or Incorrect?, Page 5

- A multiband coupler will have reduced matching at both the top and bottom of the frequency range.
 - *Yes!*
- A coupler in a radio that is specified to match 3:1 SWRs matches all 3:1 SWRs and not much else.
 - *No!*
- Couplers do not exist at VHF and above.
 - *No, but construction is done with transmission line sections and not lumped components.*

Does Coupler Use = Incompetency?

- Chest pounding by some would imply so.
 - I don't need a tuner since my antennas are designed properly. Tuners have too much loss. Idiots abound!
- A coupler is one of many tools that can be used.
- Couplers are more popular today than ever.
 - Covenants, small lot sizes, 11 HF bands (inc. 6m), etc.
 - The issue of stealth and camouflaged antennas could easily be another talk.

Choices?

- You don't have antennas to cover all desired frequencies with an acceptable SWR for your equipment.
 - Do nothing and just don't operate on some frequencies.
 - Lack of knowledge point of view. Most common and probably best if there are frequent antenna changes!
 - Estimating the impedance(s) needed to match by analysis or tables.
 - Knowing very closely the impedance(s) needed to match by measurement.

What do you really want/need?

- Matches nearly everything?, Match = 1.0:1 SWR?
- Improve SWR bandwidth?, Hardly ever adjusted?
- Peak/average power (mfg. ratings not reliable)?
- Adjust at low power?, Adjust at full power?
- Adjusts or can be adjusted very quickly?
- 160-10m, 80-10m, 6m, single band?
- Harmonic or band pass filtering?, Static bleed?
- Remotable?, Some combination of the above?

Matching Network Components

- Generally constructed from reactive components.
 - Exceptions: transmission lines, delta match, resistances such as the 800-900 Ω resistor in the B&W terminated folded dipole, etc.
- Why reactive components?
 - Reactive components with high unloaded Qs do not dissipate much power.
 - However physically large components have reduced ranges and more stray inductance and capacitance.
 - Transmission line components $\sim Q=100$.

DIY Coupler

- In approximate order of ascending cost
 - 1) Fixed inductor
 - 2) Small value fixed capacitor
 - 3) Air variable capacitor
 - 4) Air differential capacitor
 - 5) Large voltage fixed capacitor
 - 6) High voltage/current switch
 - 7) Vacuum variable capacitor
 - 8) Roller inductor

Types of Tuners

- Auto, semi-auto, manual adjust, or fixed.
- Variable, switched, and/or fixed components.
- Is coupler part of transmitter or antenna?
 - If part of the antenna then changing transmitters easy.
- Included balun, antenna switch, dummy load etc.
- Power rating and matching range. Total BS!
- Coupler/antenna as a system (military & aircraft).
- No mention yet of coupler topology.

Tying it all together

- Reflection Coefficient: $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$ $\rho = |\Gamma|$ $0 \leq \rho \leq 1$ $\rho = \frac{SWR - 1}{SWR + 1}$
- SWR: $SWR = \frac{1 + \rho}{1 - \rho}$ $\rho = \sqrt{\frac{(R_L - R_0)^2 + (X_L)^2}{(R_L + R_0)^2 + (X_L)^2}}$
- Return Loss: $RL_{dB} = -20 \times \log_{10}(\rho)$ $P_{Ref} = P_{Fwd} \times \rho^2$
- Mismatch Loss: $P_{Load} = P_{Fwd} - P_{Ref}$

$$ML_{dB} = -10 \times \log_{10} \left(\frac{P_{Fwd} - P_{Ref}}{P_{Fwd}} \right) = -10 \times \log_{10} (1 - \rho^2)$$

SWR	ρ	Return Loss (dB)	Mismatch Loss (dB)	Power To Load ¹
1.1	0.05	26.44	0.01	100%
1.2	0.09	20.83	0.04	99%
1.5	0.20	13.98	0.18	96%
2	0.33	9.54	0.51	89%
2.5	0.43	7.36	0.88	82%
3	0.50	6.02	1.25	75%
5	0.67	3.52	2.55	56%
10	0.82	1.74	4.81	33%
20	0.90	0.87	7.41	18%
50	0.96	0.35	11.14	8%

Note 1: Does not include additional loss in transmission line due to SWR or any fold back in transmitter.


Voltages and Currents

$$V_{pk} = \sqrt{2 \times P \times R_o}$$

$$V_{pk} \leq \sqrt{2 \times P \times R_o \times SWR}$$

$$I_{rms} = \sqrt{\frac{P}{R_o}}$$

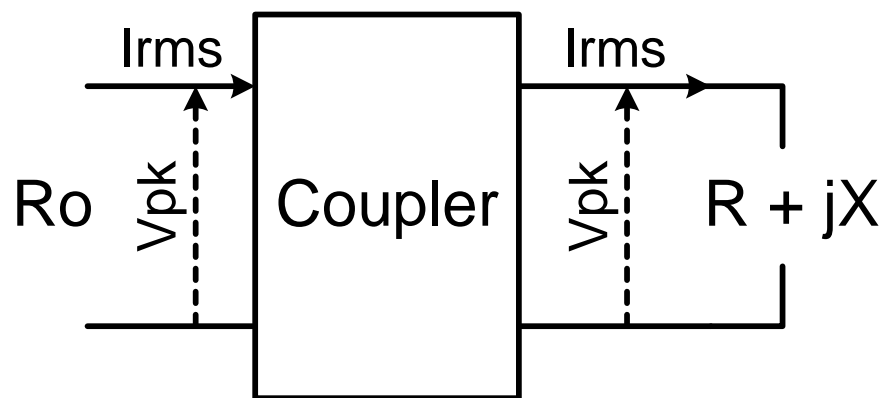
$$I_{rms} \leq \sqrt{\frac{P \times SWR}{R_o}}$$



SWR	Power	Vpk(max)	Irms(max)
1:1	100W	100V	1.41A
	1500W	387V	5.48A
3:1	100W	173V	2.45A
	1500W	671V	9.5A
10:1	100W	316V	4.47A
	1500W	1225V	17.3A
20:1	100W	447V	6.32A
	1500W	1732V	24.5A
50:1	100W	797V	10.0A
	1500W	2739V	38.7A

Stresses Within the Tuner @ 1500W

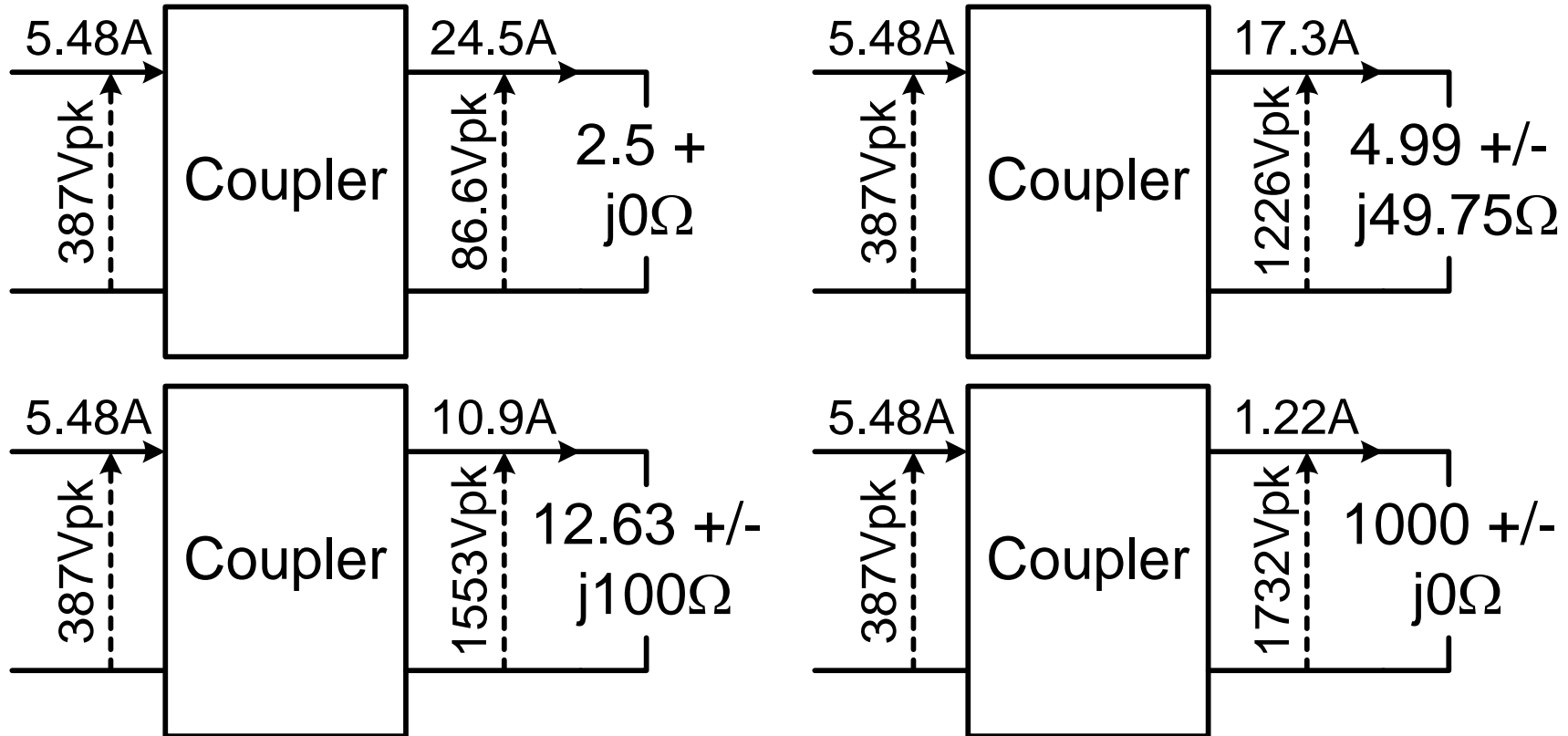- All are 20:1 SWRs. Stresses & losses are different.




“Small” Antenna Examples

- Example#1
 - 1.8MHz using 40m (67.2') dipole, 50' high, #12 Cu wire
 - $Z = 1.60 - j2420$ (SWR ~73000:1)
 - $I_{rms} = 30.6A$ (1500W), $V_{pk} = 104.7kV$
- Example #2
 - 1.8MHz using 80m (135') dipole, 50' high, #12 Cu wire
 - $Z = 5.9 - j1080$ (SWR ~3950:1)
 - $I_{rms} = 15.94A$ (1500W), $V_{pk} = 24.3kV$
- No tuners match these impedances well!
- A little loss is desperately needed.


What is the Smith Chart

- A polar plot of the reflection coefficient including phase.
- This results in:
 - Plots of constant SWRs are circles.
 - Inductive impedances are above the center line.
 - Capacitive impedances are below the center line.
 - The horizontal axis goes from 0Ω at the far left to R_0 at the center to infinity at the far right.

Smith Chart Regions

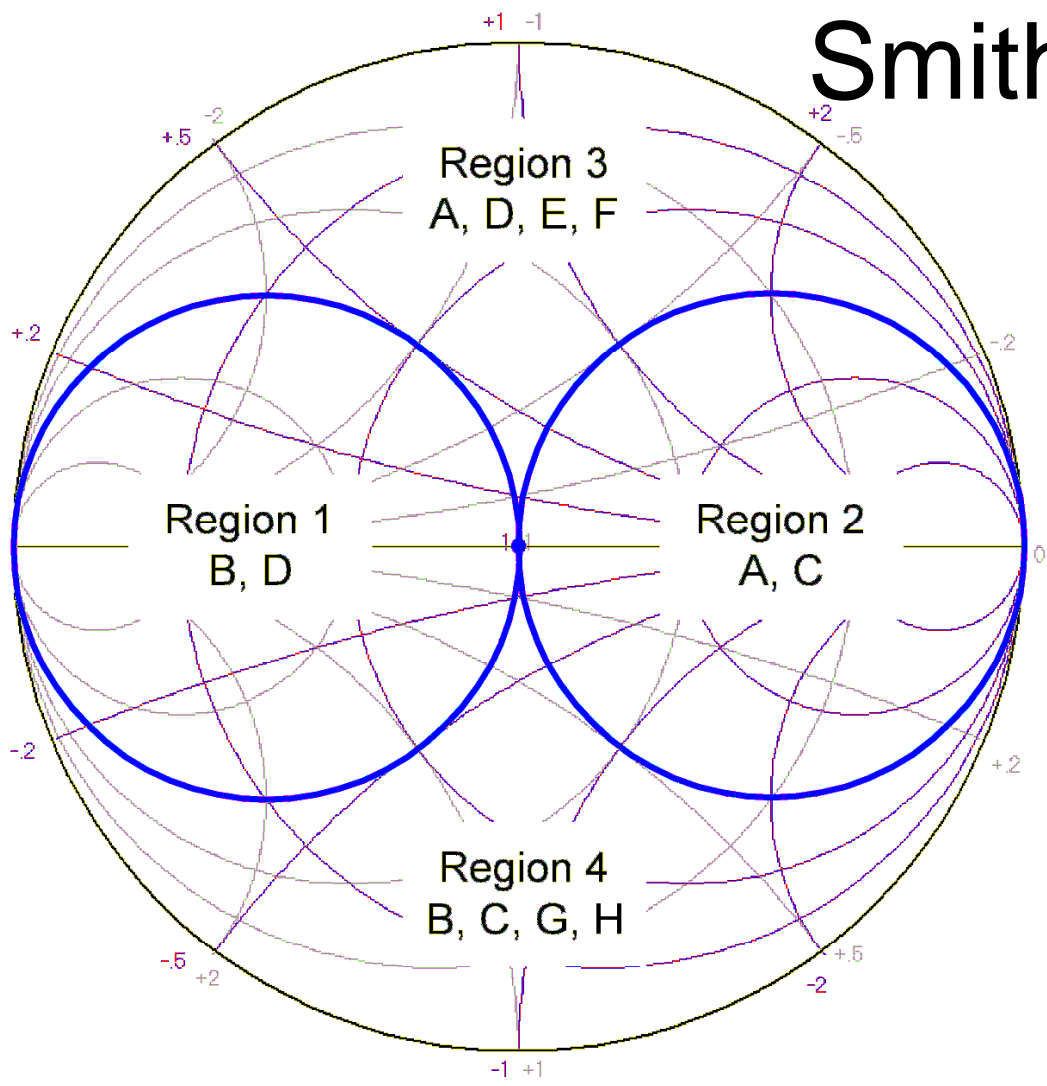

L type circuits

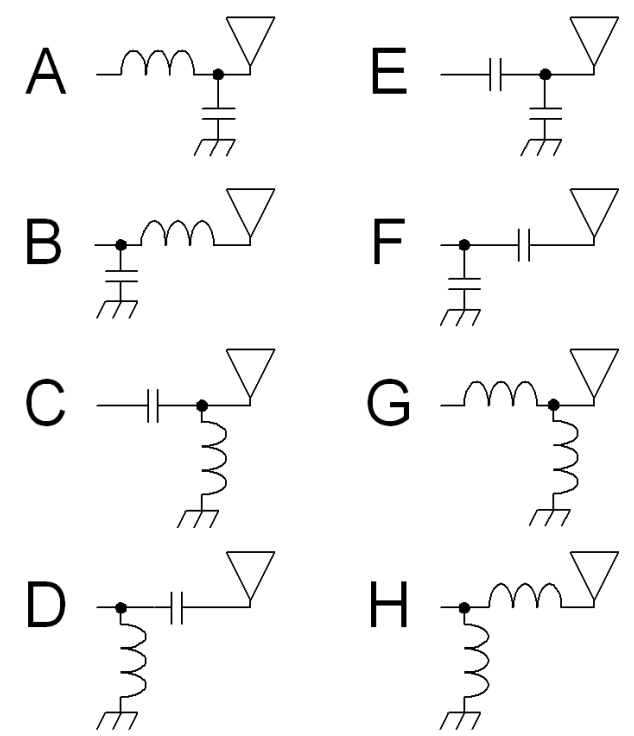


Example Smith Chart showing SWR circles

5:1 = Green

10:1 = Red

20:1 = Orange

$50 + j0$ (SWR = 1:1)

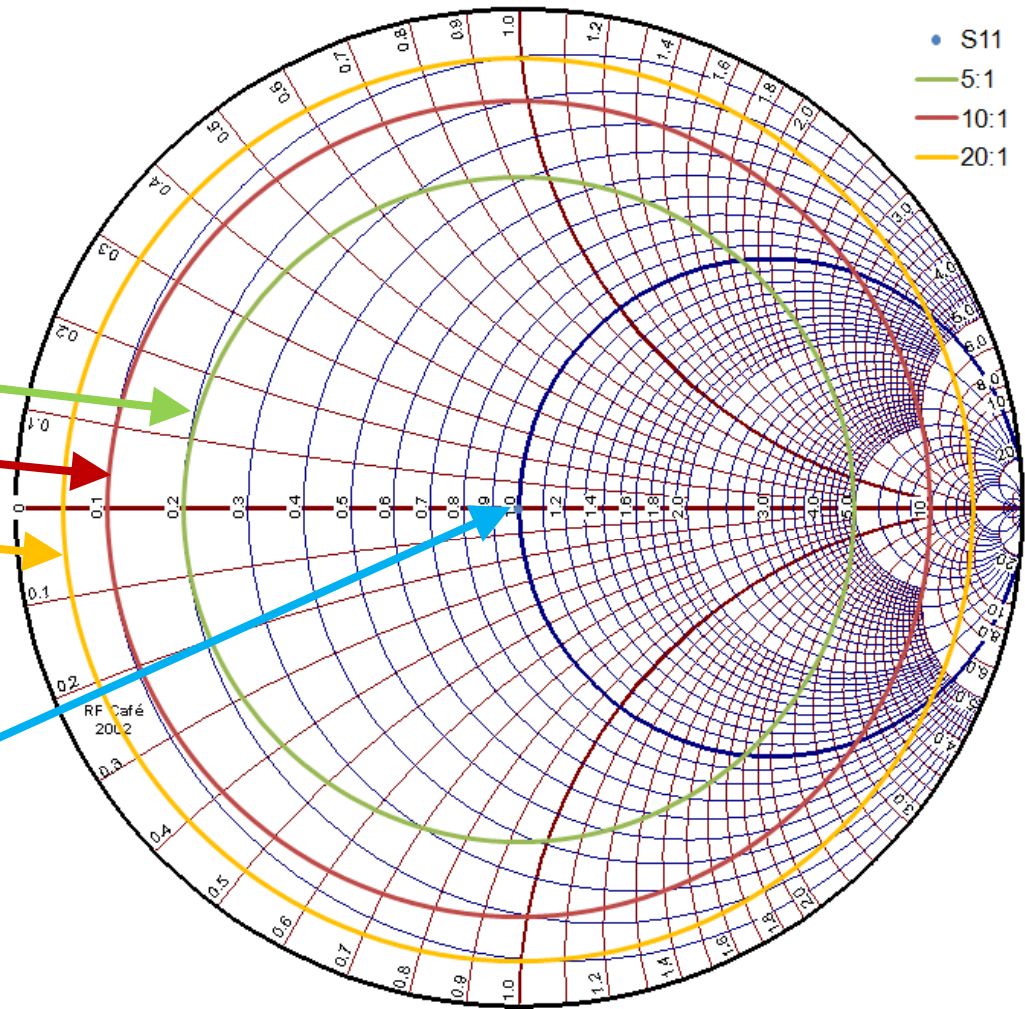

Matching Range Simulator
Swing SWR Circles



XX MHz

Sample Design Goals

- Match all SWRs of at least 20:1 from 160m thru 20m with reduced SWRs up thru 6m.
- Do the basic design on 40m realizing that 4X more C & L will be needed on 160m etc.
- Ignore stray C & L for now.
- Explain old Johnson Matchbox with open wire line and large antennas vs today's use of a coupler.

Low Pass "L" Network Type "A"

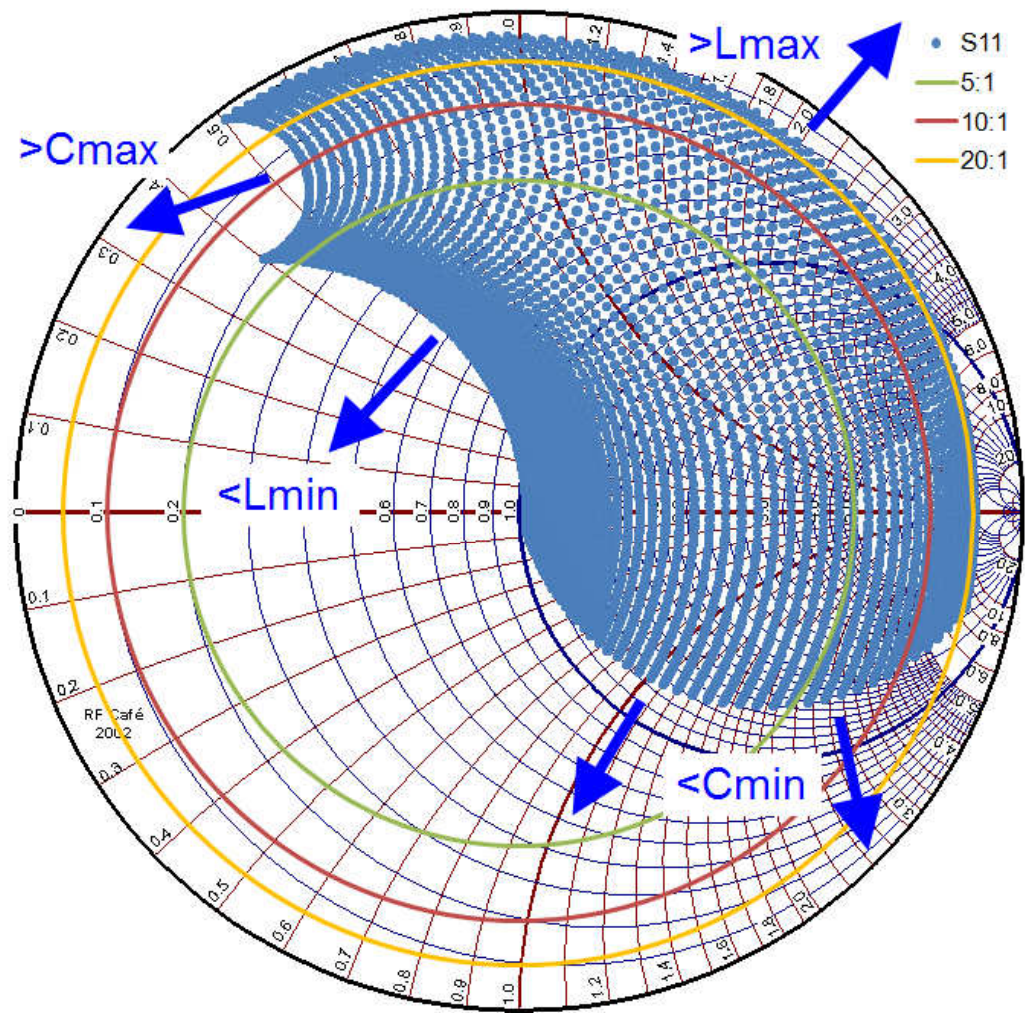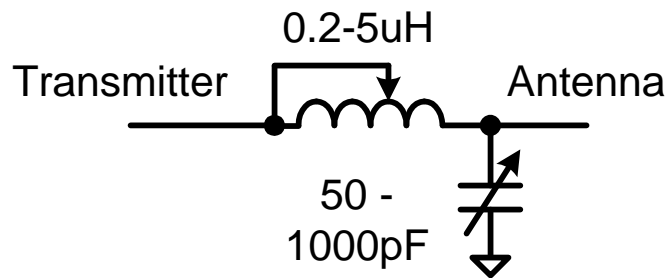- Shunt "C" on ANT Side
- Series "L"
- Need $>C_{max}$ & $<C_{min}$





Low Pass "L" Network
"Lseries-Cshunt"

7 MHz

Low Pass "L" Network Type "B"

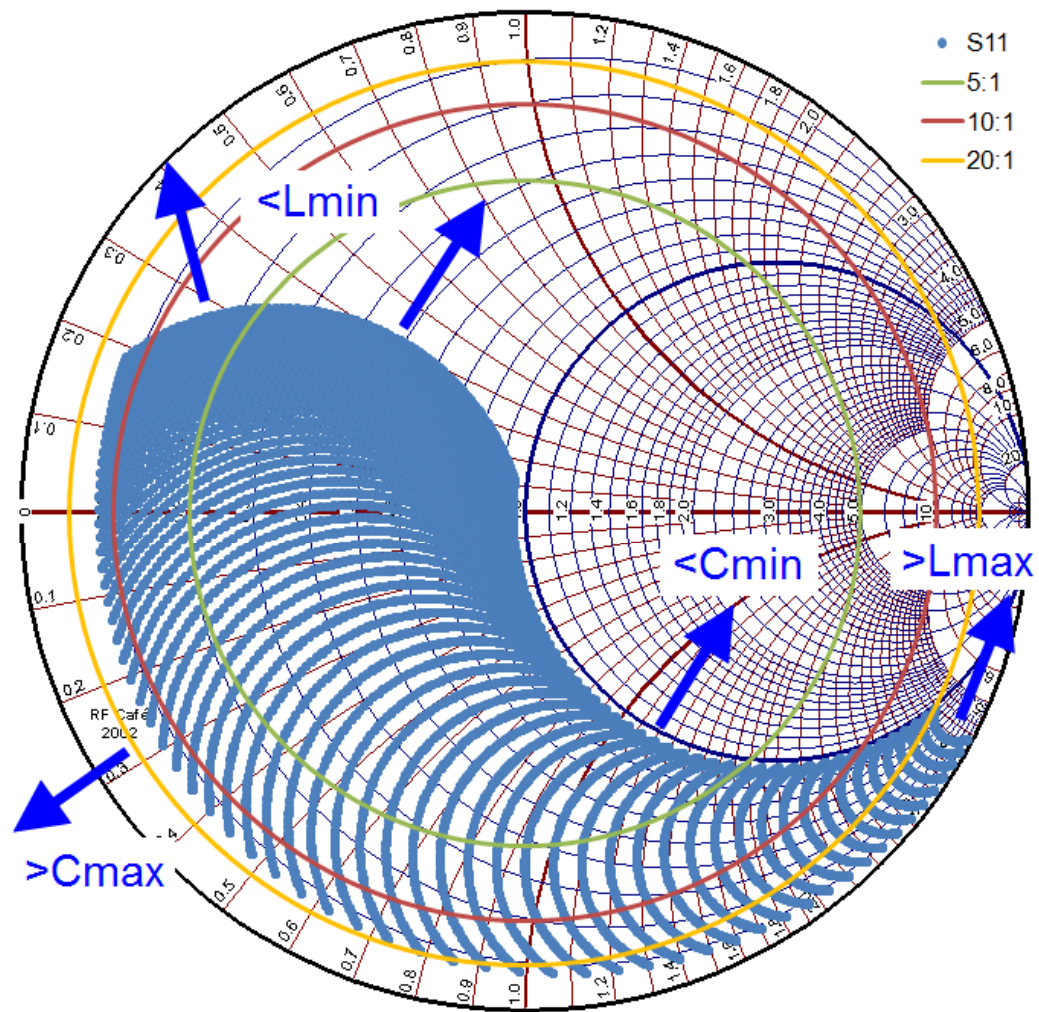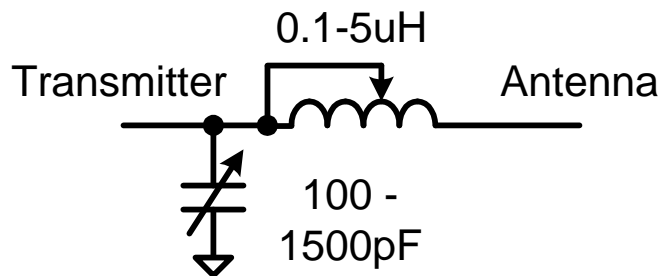- Shunt "C" on TX Side
- Series "L"
- Need $<L_{min}$ & $>C_{max}$



Low Pass "L" Network
"Cshunt-Lseries"



7 MHz

Low Pass “L” Network Results

- $C_{max} \approx 8000\text{pF}$ & $L_{max} \approx 20\mu\text{H}$ on 160m
- $C_{min} \approx 5\text{pF}$ & $L_{min} \approx .02\mu\text{H}$ on 6m
- Pretty ugly component values.
- This happens when only 2 adjustable components, wide frequency, & wide matching range are wanted.
- Need some switchable offset components or variable offset components to help match especially on the higher frequencies.



High Pass "L" Network Type "C"

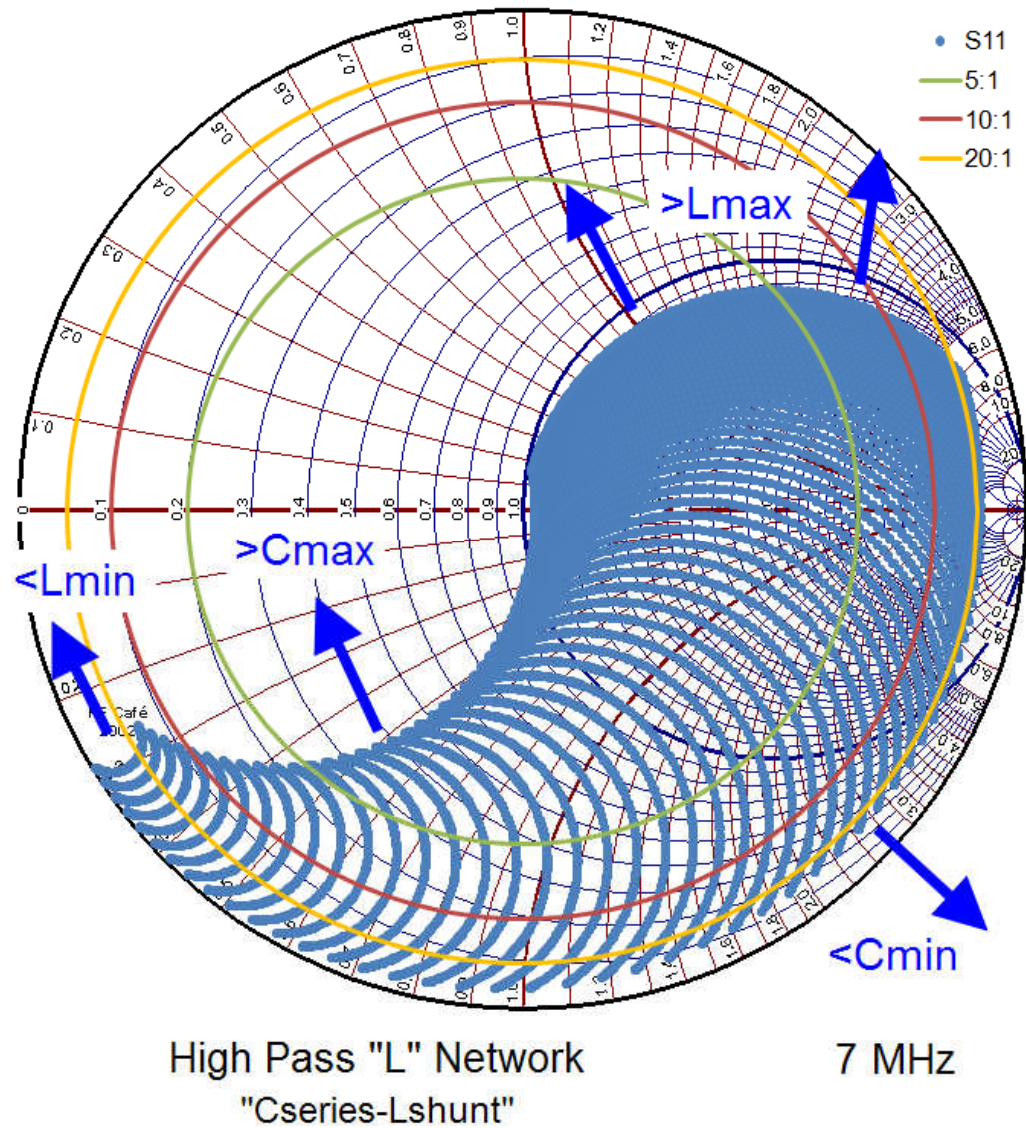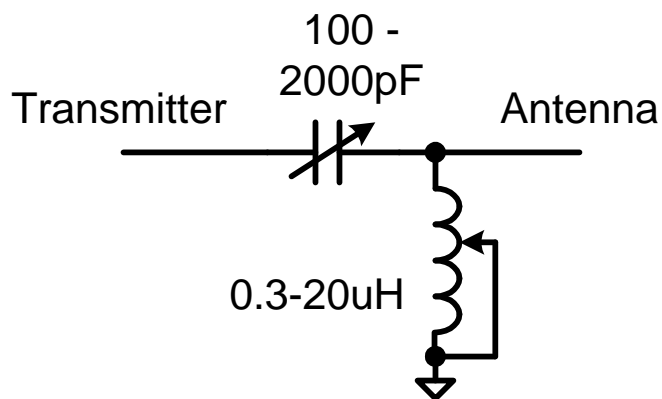- Shunt "L" on ANT Side
- Series "C"
- Need $>L_{max}$ (not good)



High Pass "L" Network Type "D"

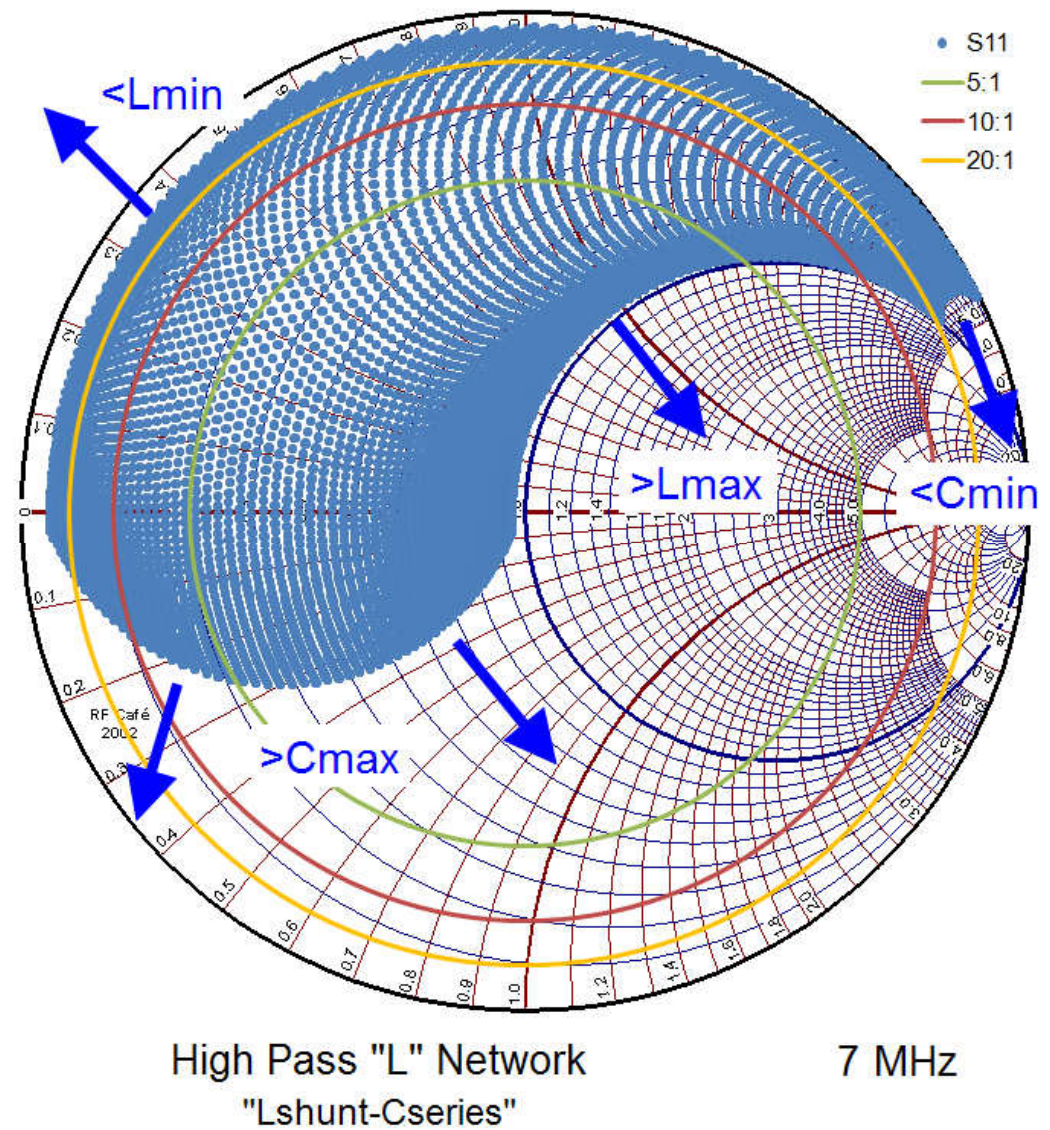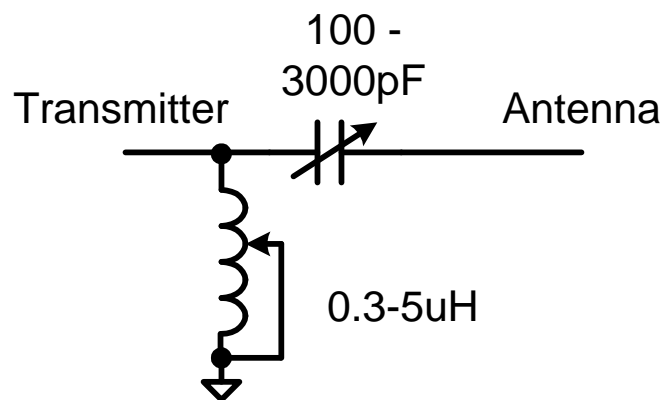- Shunt "L" on TX Side
- Series "C"
- Need $>C_{max}$ (not good)



High Pass “L” Network Results



- Worse component values than Low Pass “L”.
- Variable component “L” networks are not commonly used for wide range matching on the lower frequencies for good reason.
- Low Pass “L” networks are used in most switched component tuners with reduced 160m & 80m matching range.
- Often good choice if match impedance is known.

Adding a 3rd Component

- Does adding a 3rd adjustable component help the matching range?
- Could the Low Pass “Pi” could be this network?
- A “Pi” network is still a 2 terminal network.

Low Pass "Pi" Network

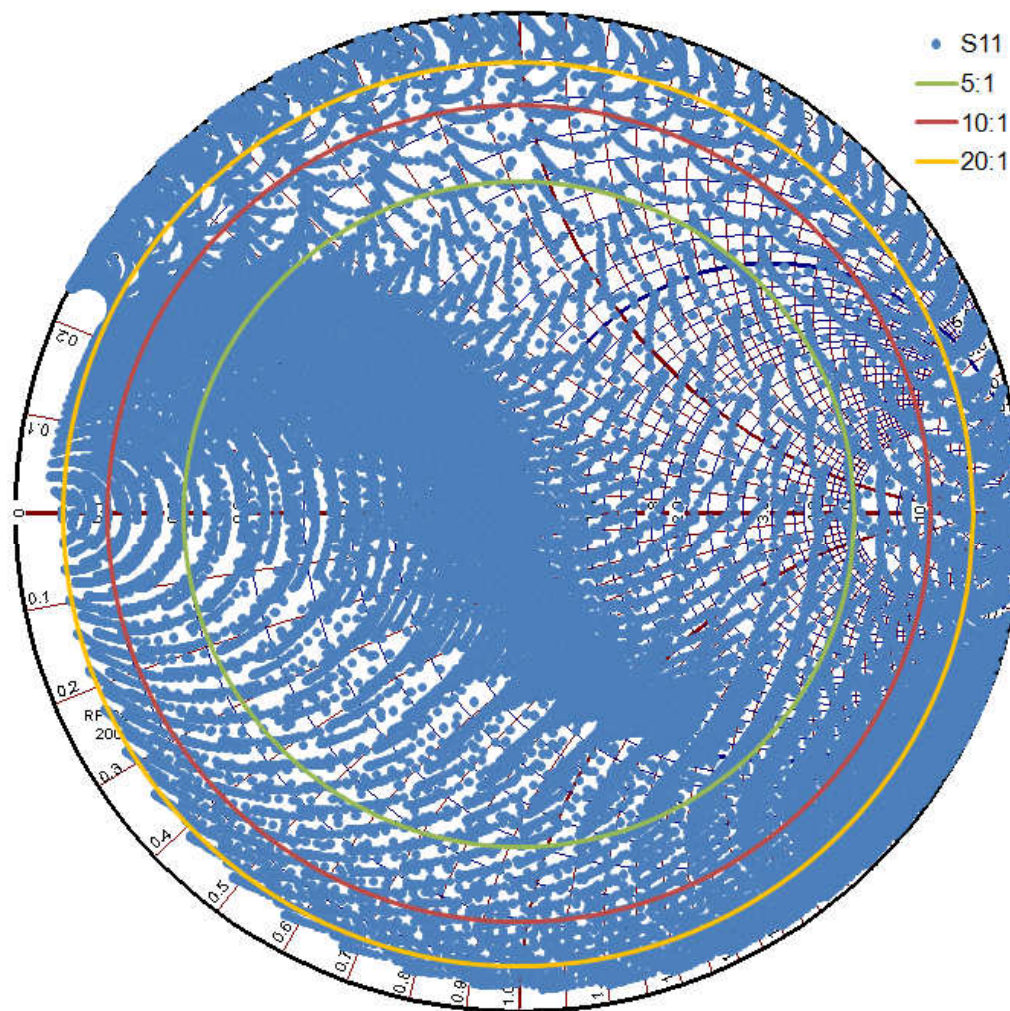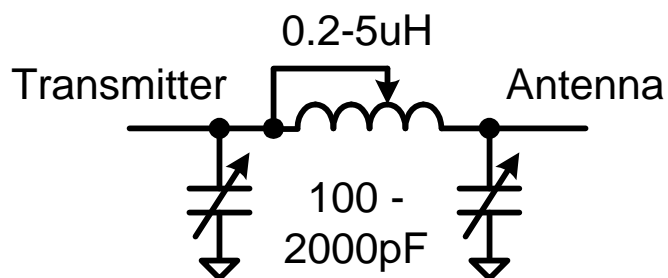- Great matching range
- Similar component values to the Low Pass "L" network





Low Pass "Pi" Network
"Cshunt-Lseries-Cshunt"

7 MHz

Low Pass "Pi" Network

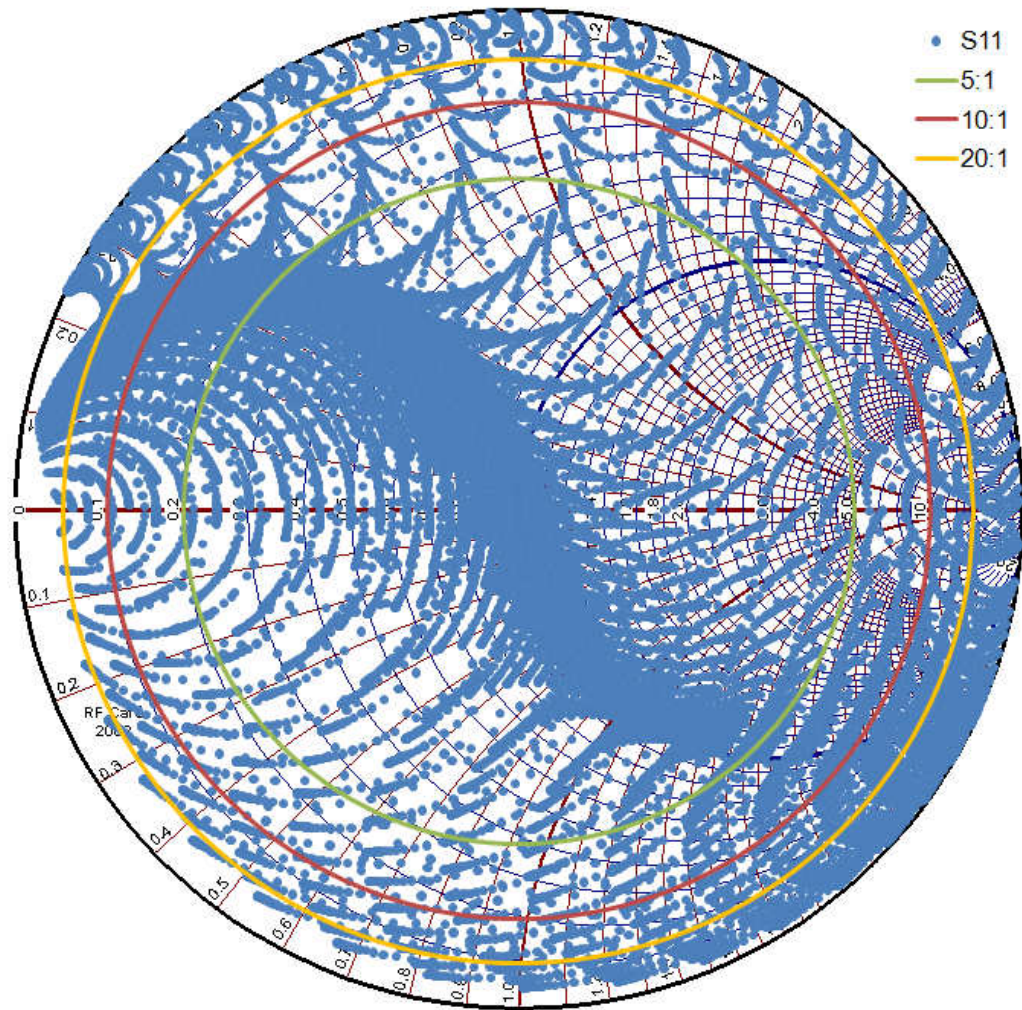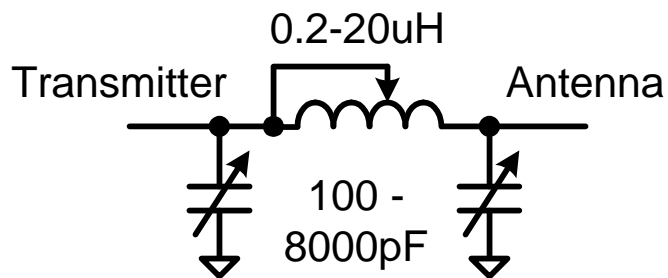- Great matching range
- Notice new scaled component values!





Low Pass "Pi" Network
"Cshunt-Lseries-Cshunt"

1.8 MHz

Low Pass "Pi" Network

- Still good matching range

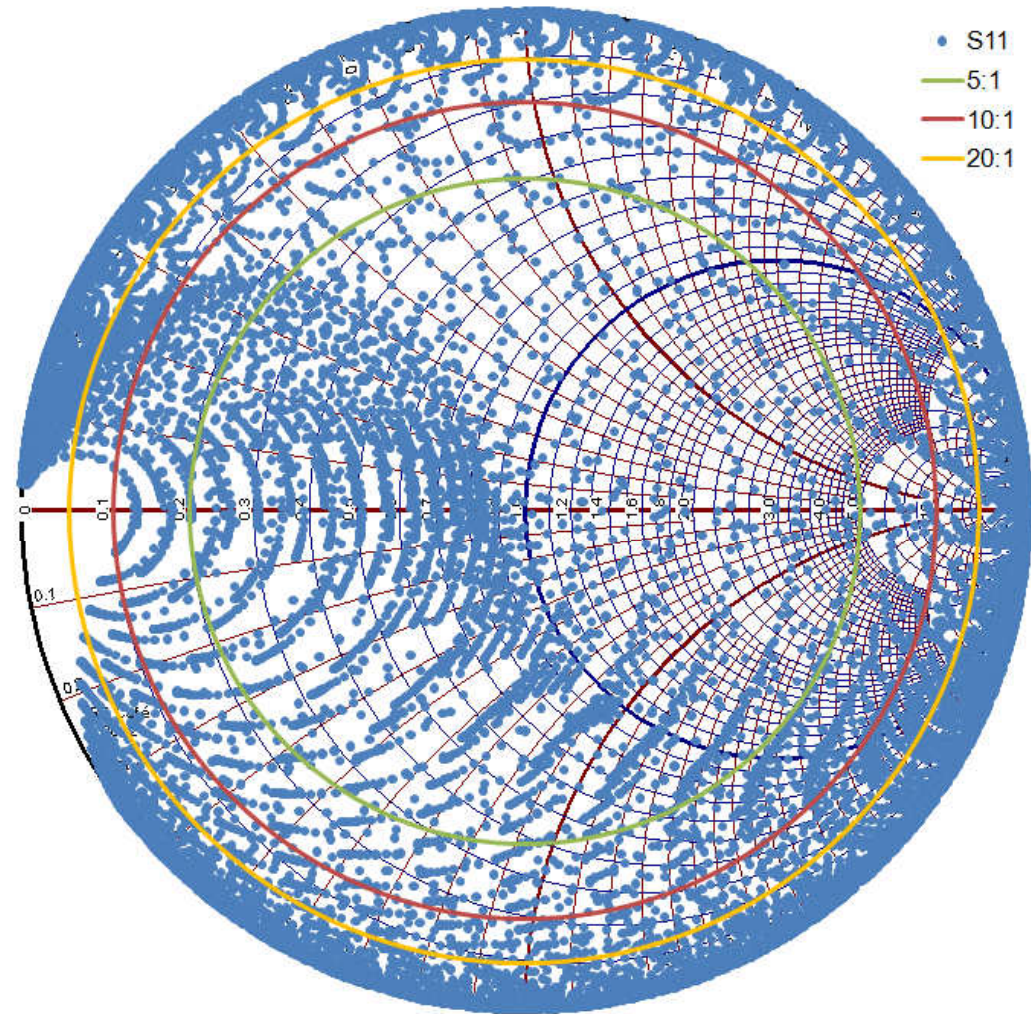
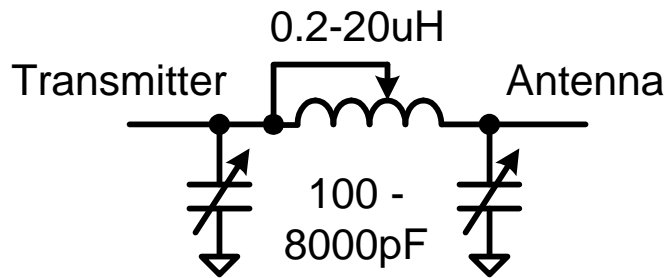


Low Pass "Pi" Network
"Cshunt-Lseries-Cshunt"

14 MHz

Low Pass "Pi" Network

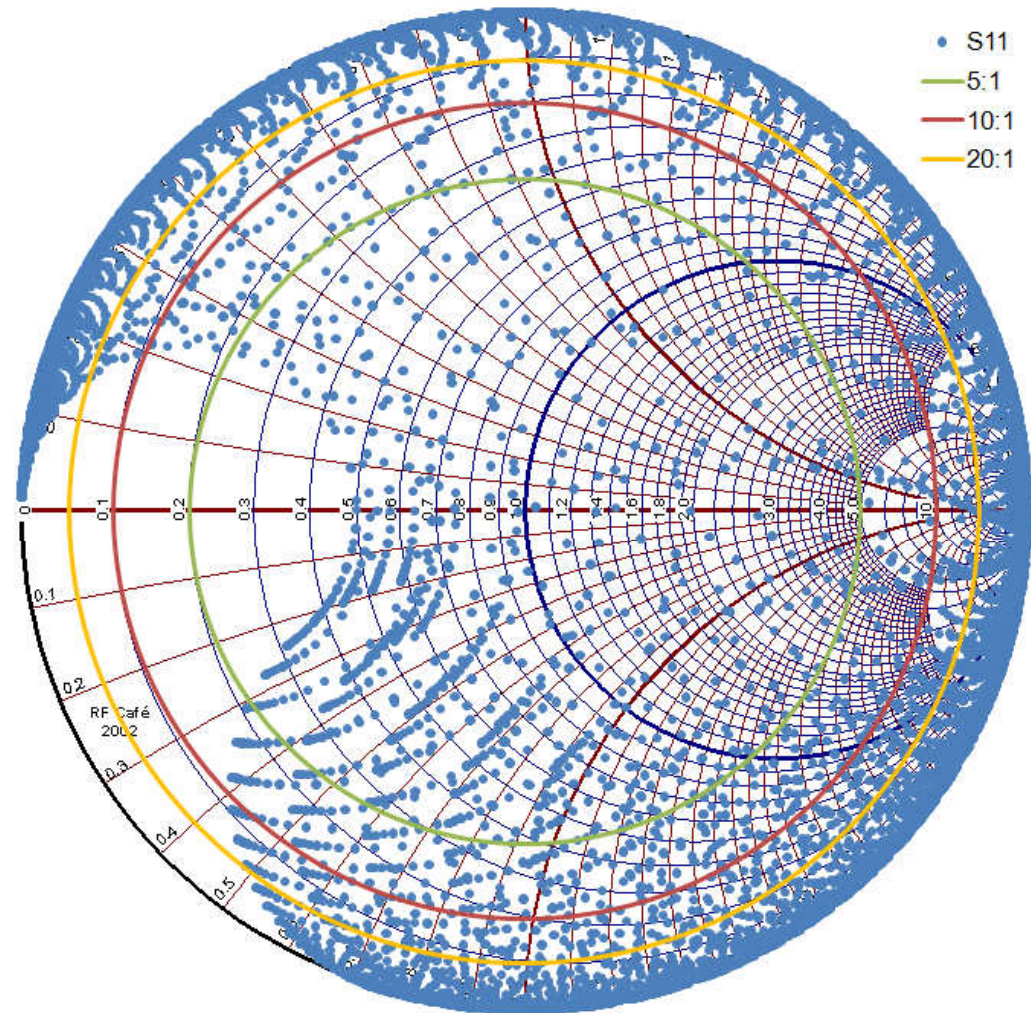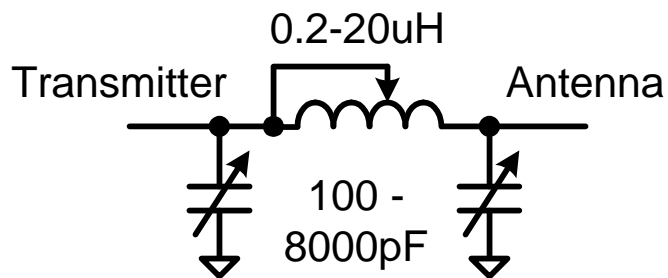- Not good matching range
- Needs $<C_{min}$ and $<L_{min}$





Low Pass "Pi" Network
"Cshunt-Lseries-Cshunt"

28 MHz

Low Pass "Pi" Network

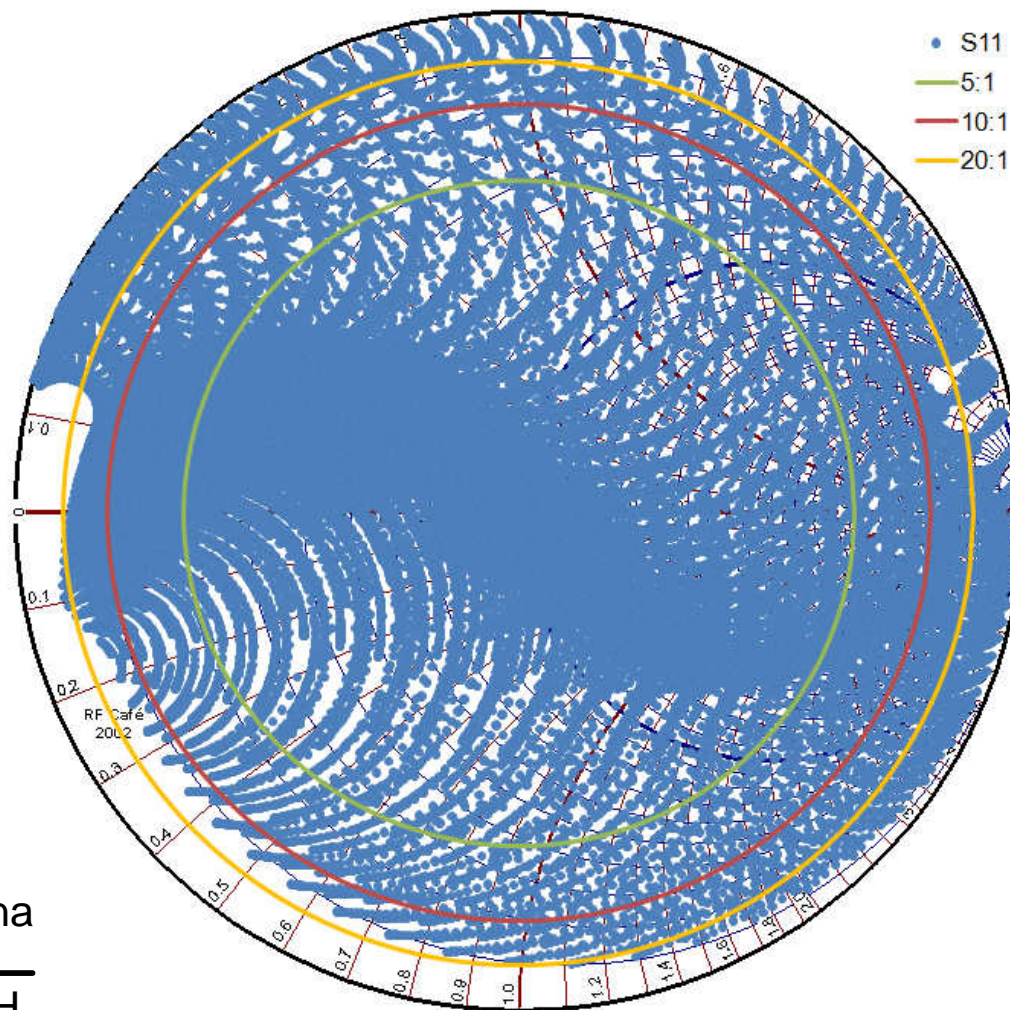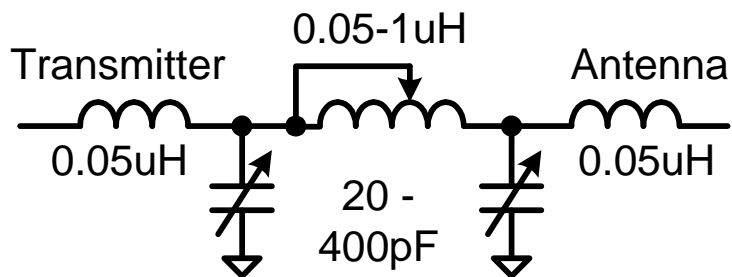- Very good matching range
- Modified for Cmin which includes stray C to Gnd
- Includes stray L on input and output





Low Pass "Pi" Network
"Cshunt-Lseries-Cshunt"

28 MHz

Low Pass "Pi" Network

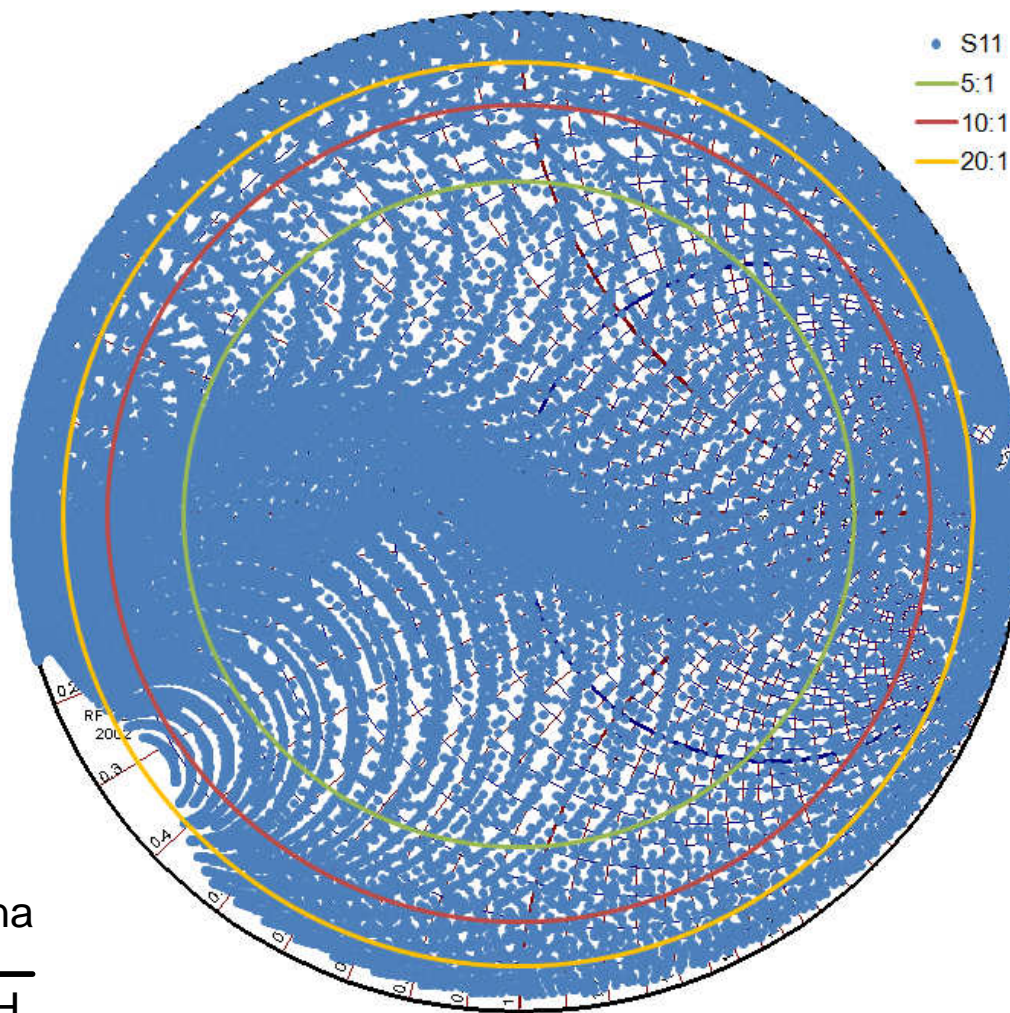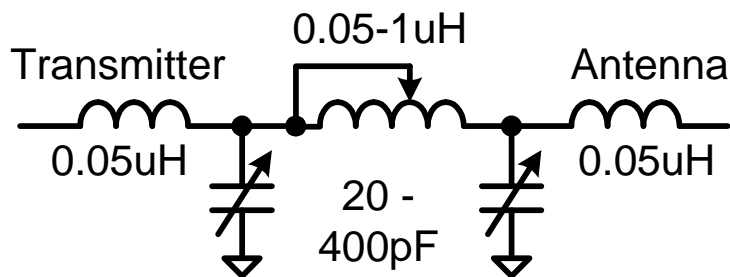- Very good matching range
- Modified for $<C_{min}$ which includes stray C to Gnd
- Includes stray L on input and output
- 6m range better than 10m due to 0.05uH



Low Pass "Pi" Network
"Cshunt-Lseries-Cshunt"



50 MHz

High Pass “Tee” Network

- Neither the “L” or Low Pass “Pi” networks seems like a good candidate for use as an all band general matching network.
- The “Tee” network has an effective 3rd node which increases flexibility at the expense of possible additional loss.
- 80-90% of any coupler loss is in the inductor(s) so improving inductor Q can offset loss concerns.

High Pass "Tee" Network

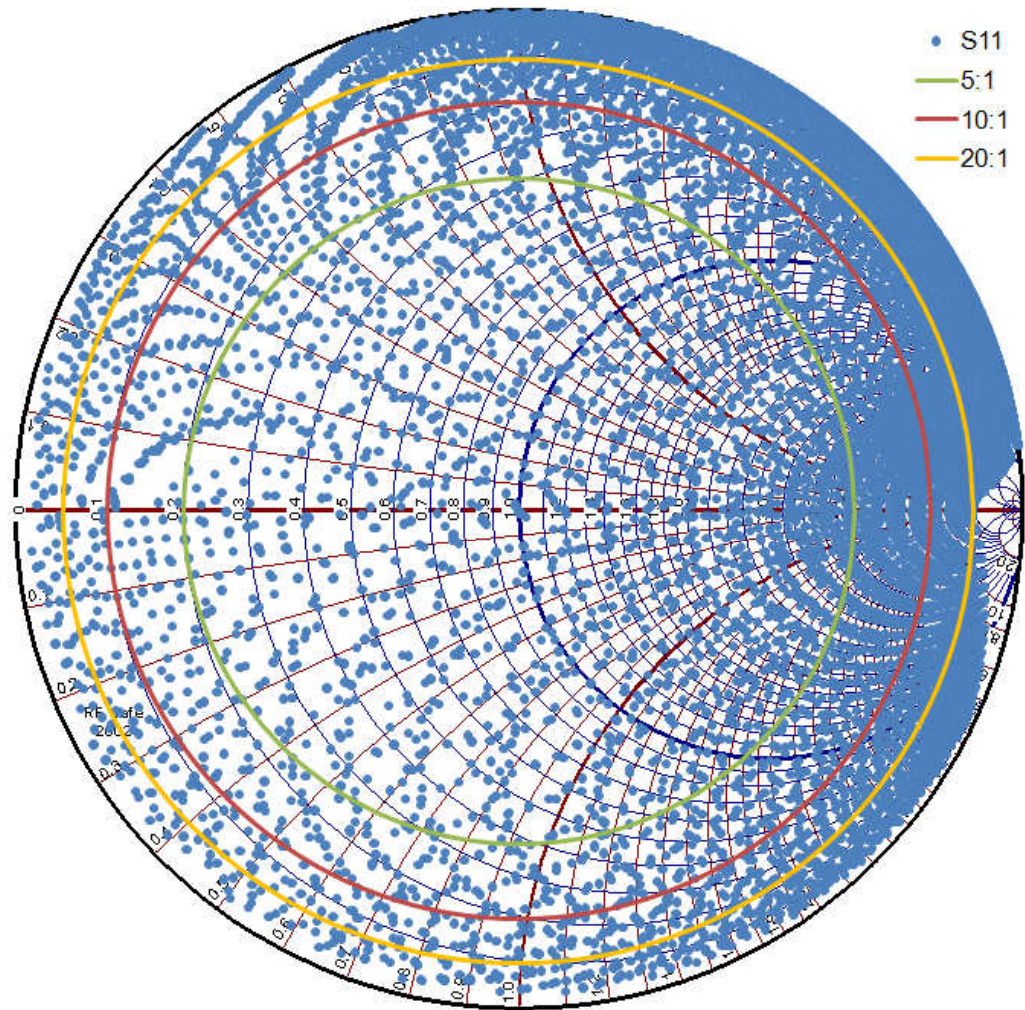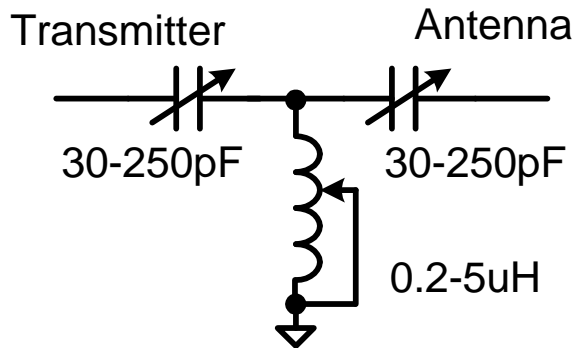- Pretty easy to see why the high pass "Tee" network is popular
- Nice component values





High Pass Tee Network
"C-L-C"

7 MHz

High Pass "Tee" Network

- Great matching range

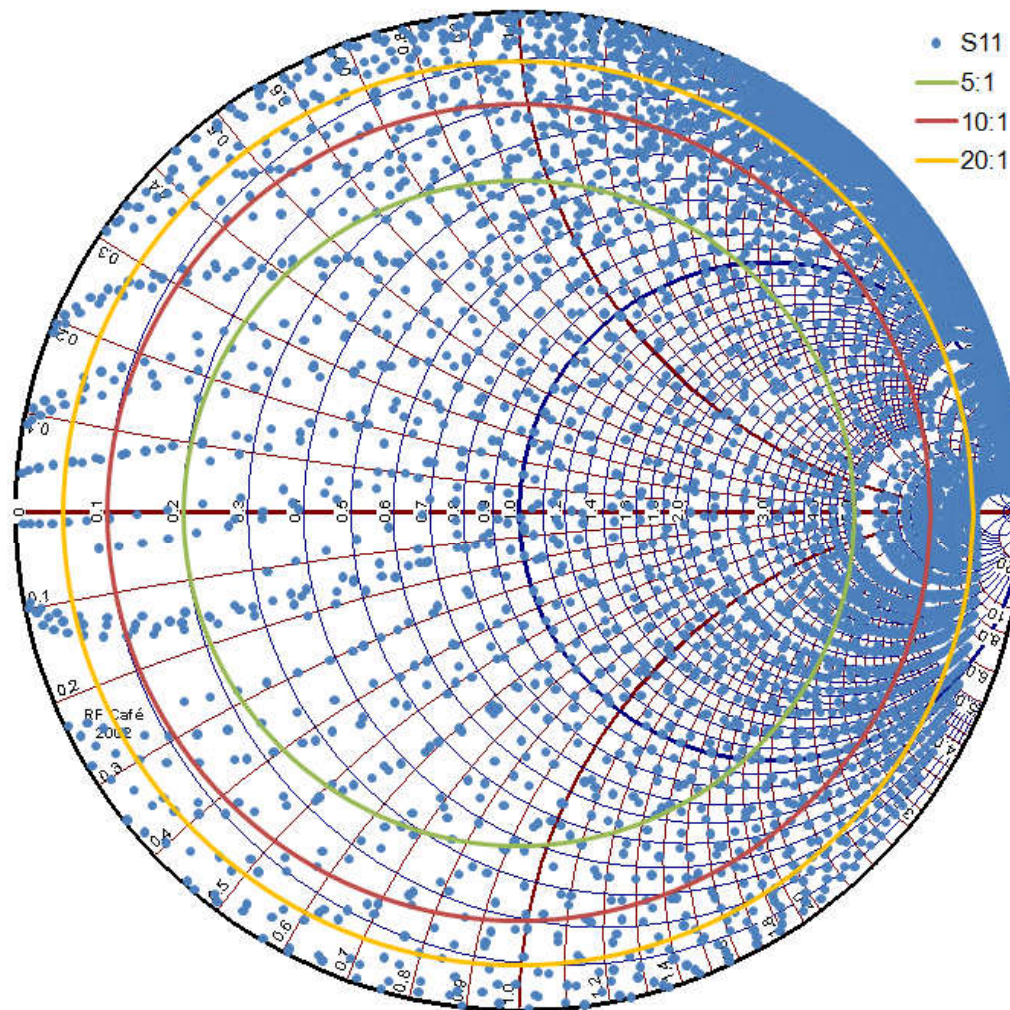
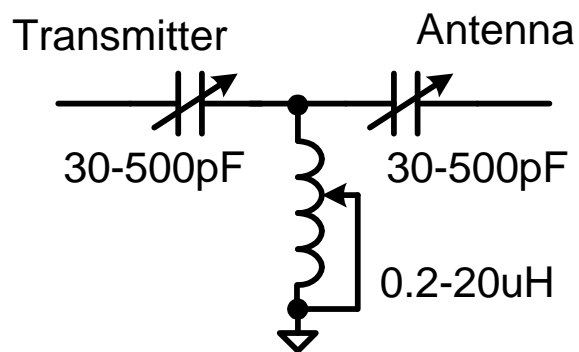


High Pass "Tee" Network
"C-L-C"

1.8 MHz

High Pass "Tee" Network

- Still great matching range

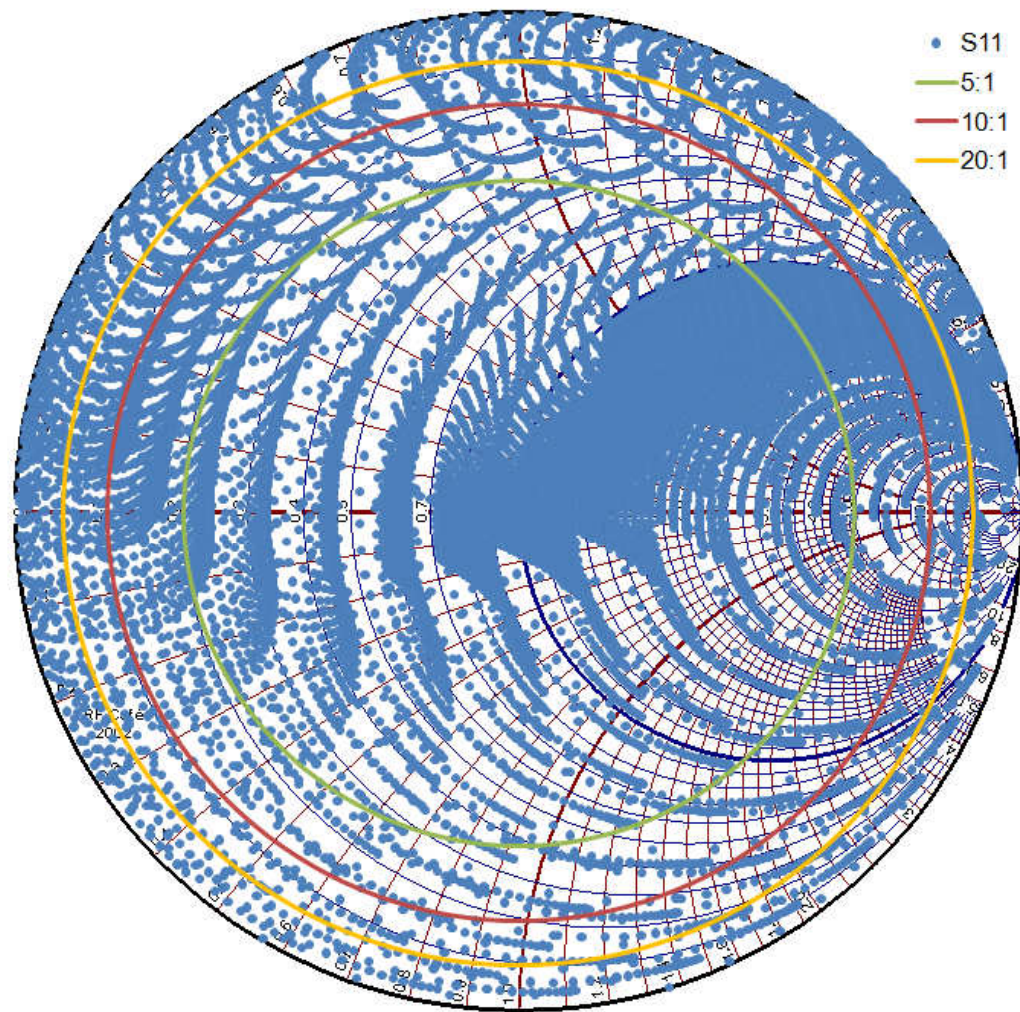
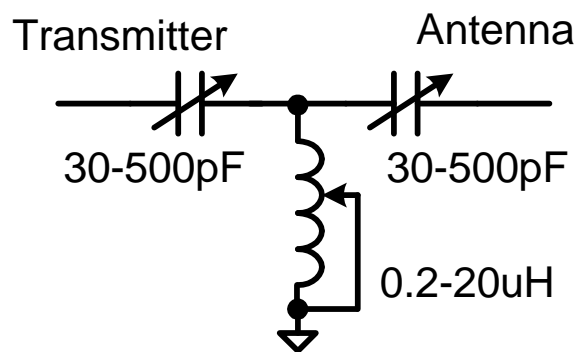


High Pass "Tee" Network
"C-L-C"

14 MHz

High Pass "Tee" Network

- Very good matching range

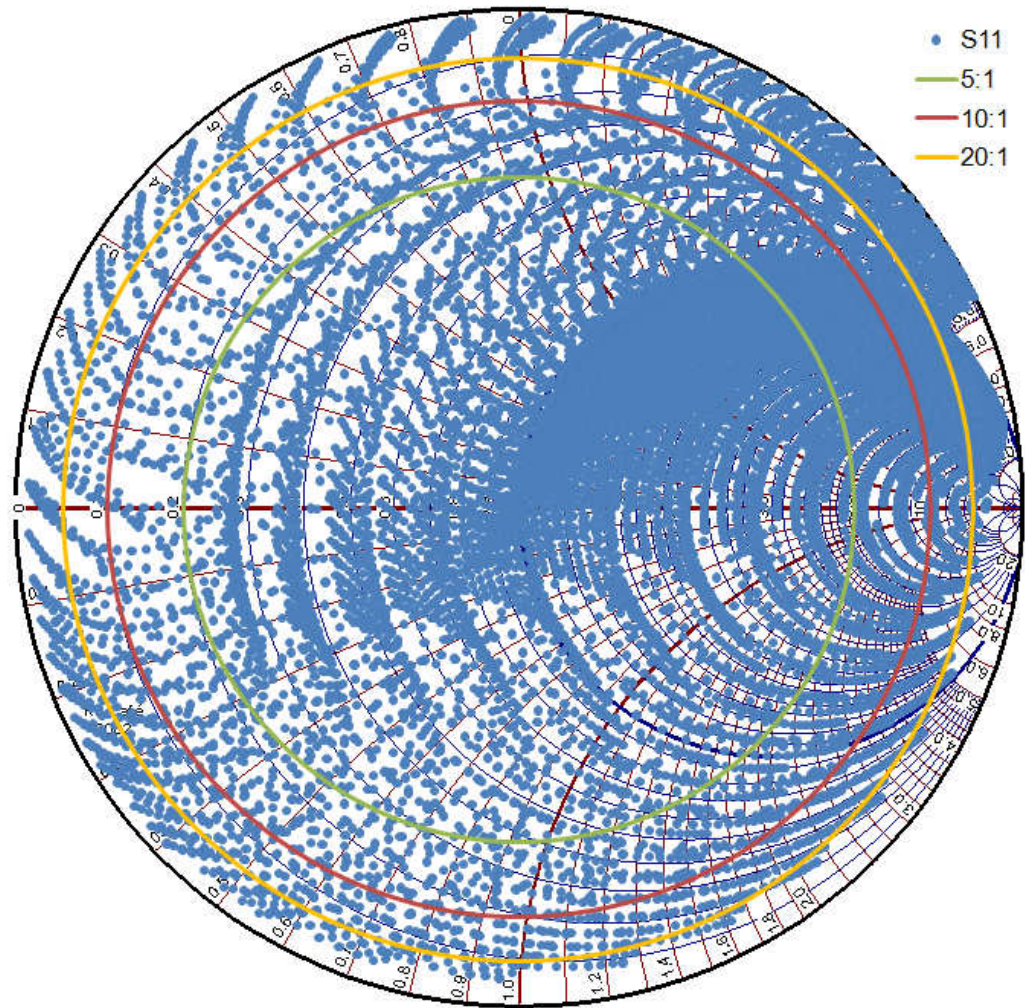
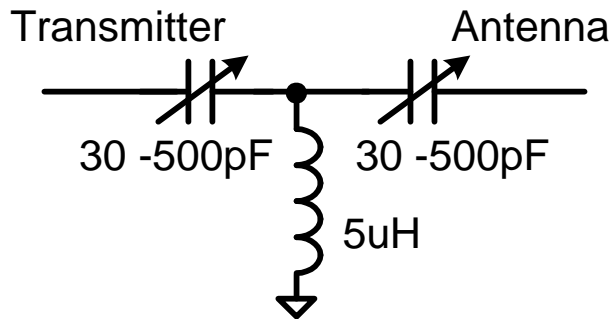


High Pass "Tee" Network
"C-L-C"

21 MHz

High Pass "Tee" Network

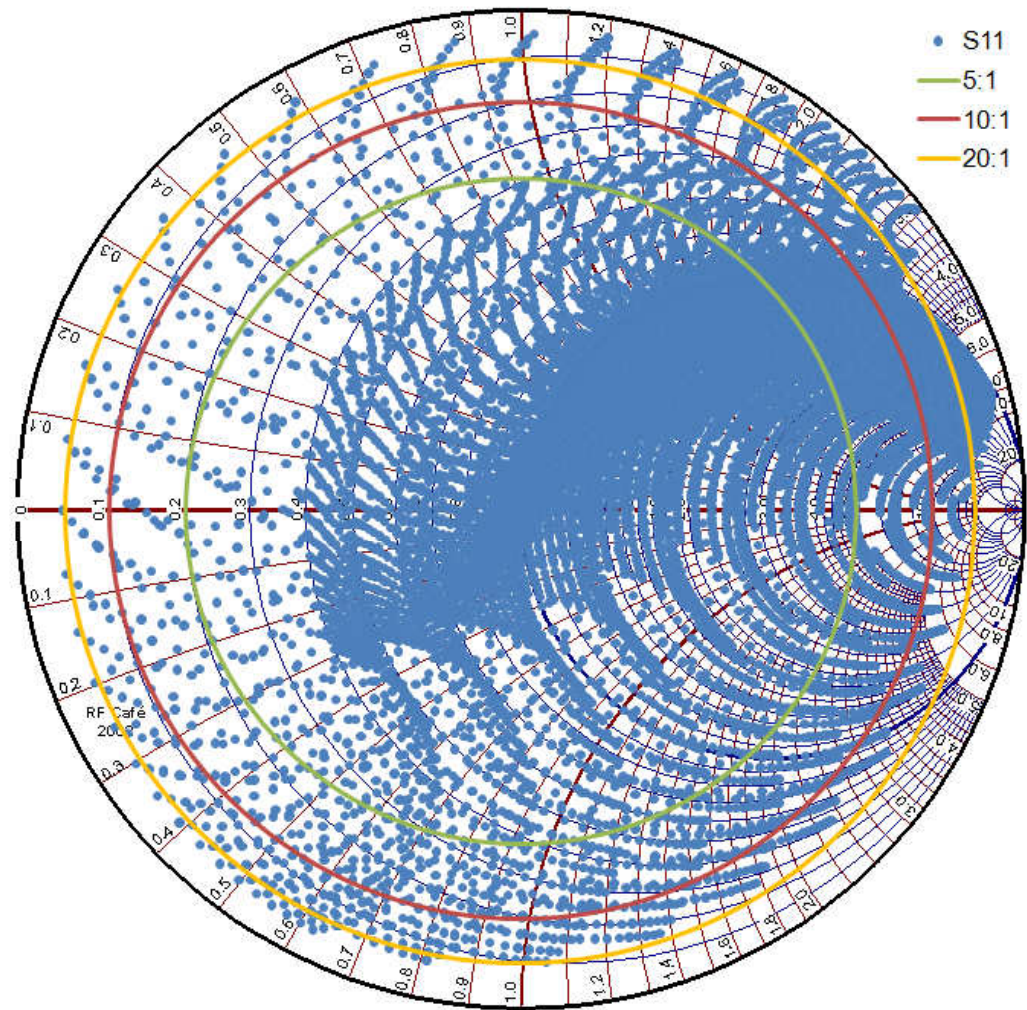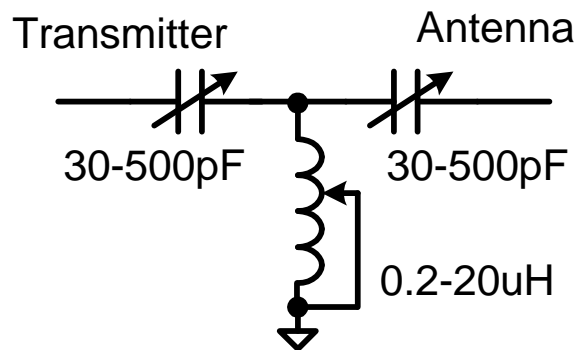- Obvious why the High Pass "Tee" is popular





High Pass "Tee" Network
"C-L-C"

28 MHz

High Pass "Tee" Network

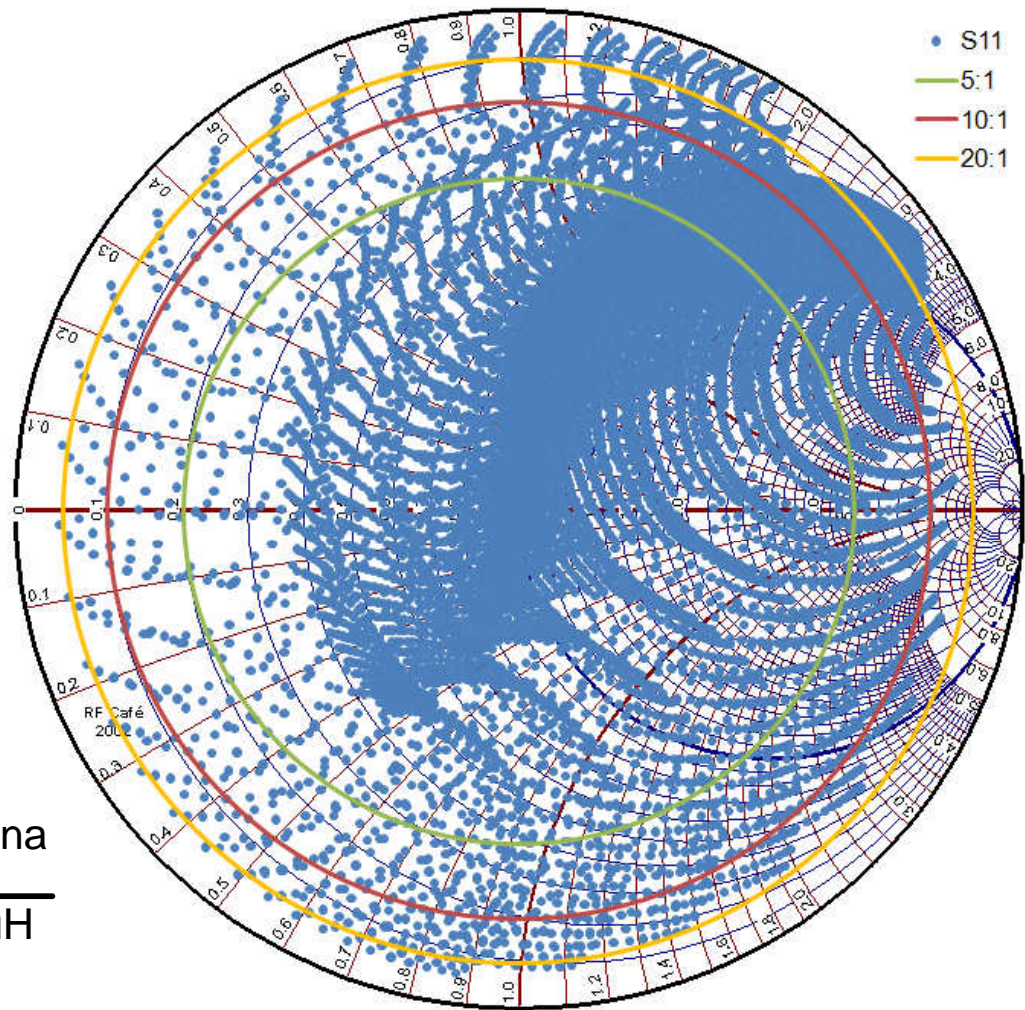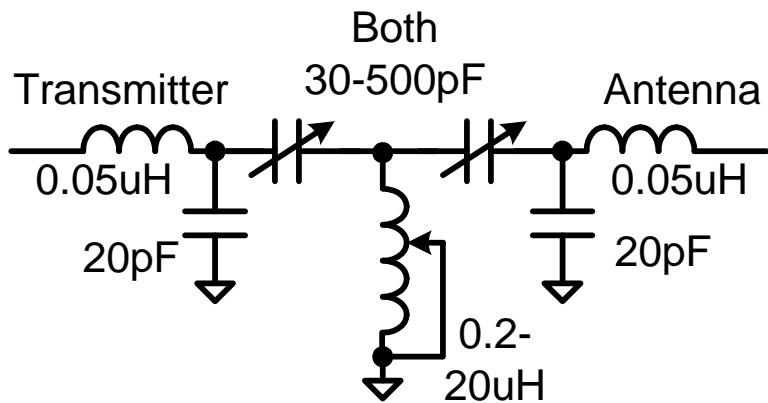- What if we include the stray Cs & Ls
- Still great matching range





High Pass "Tee" Network
"C-L-C"

28 MHz

High Pass "Tee" Network

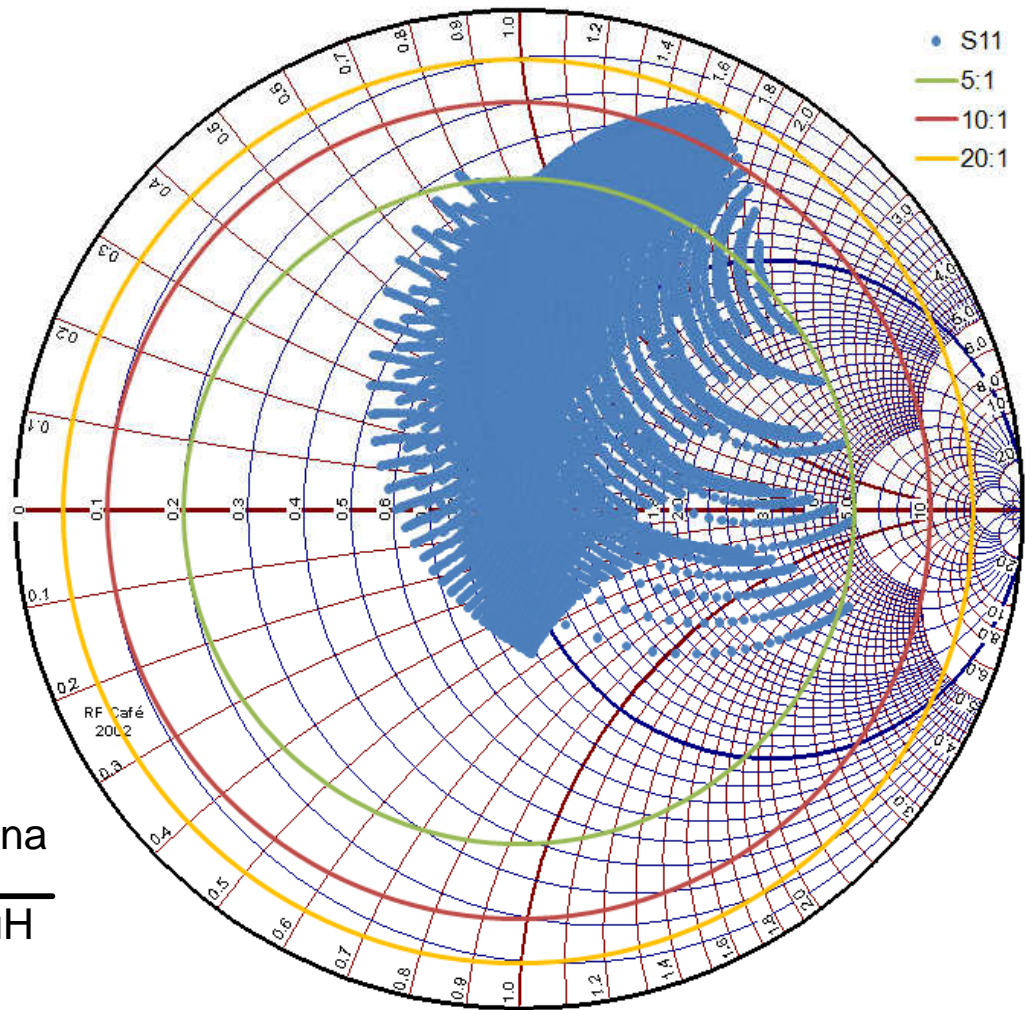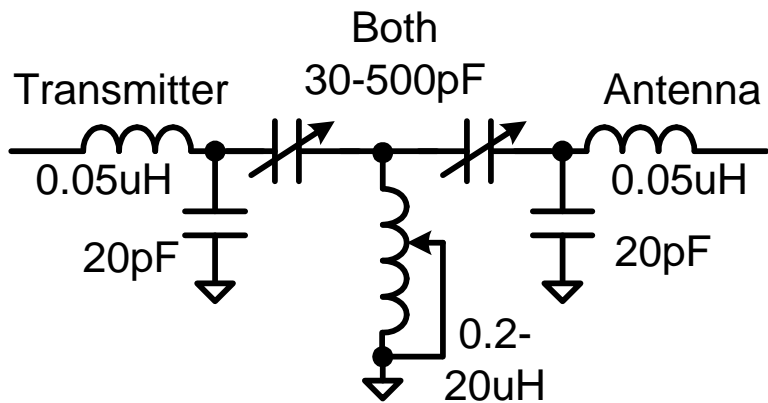- Matching range is poor
- Lmin is too large (reactance = +j63 @50MHz)





High Pass "Tee" Network
"C-L-C"

50 MHz

Fixed "L" High Pass "Tee" Network

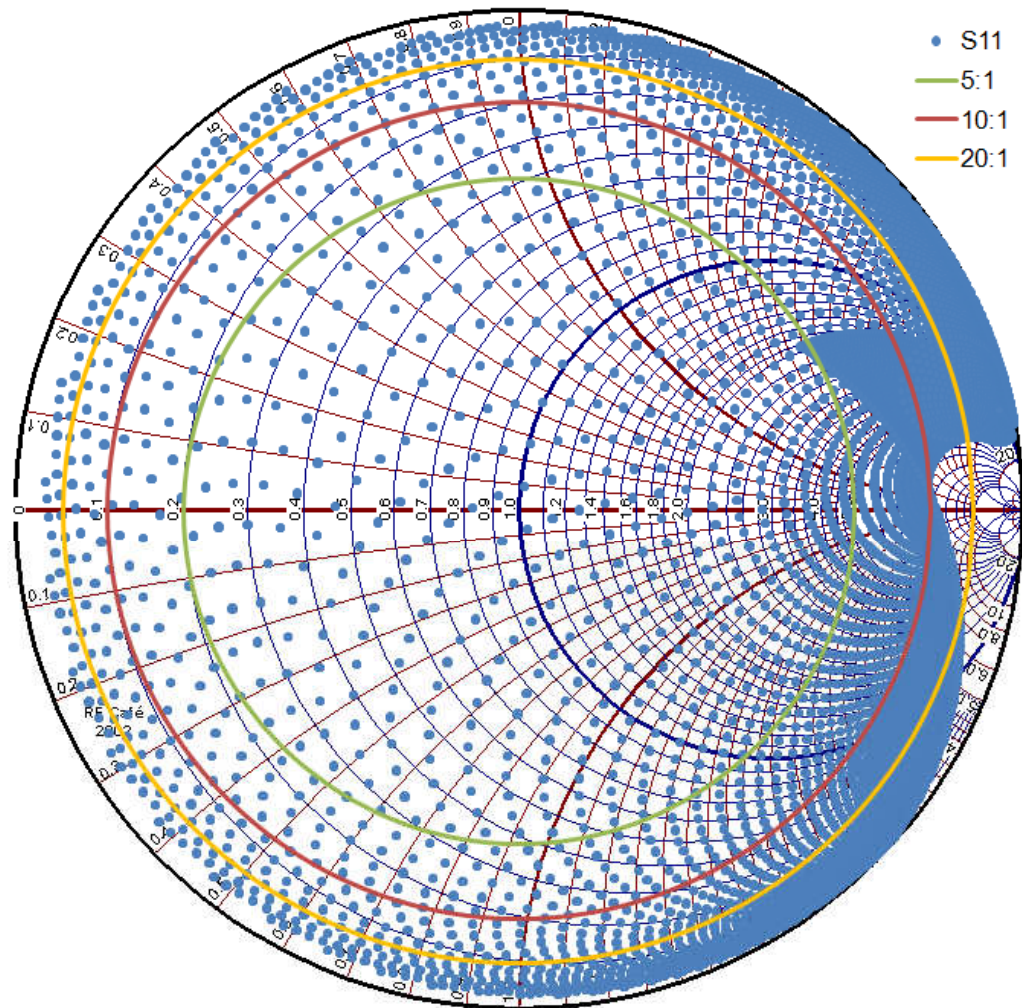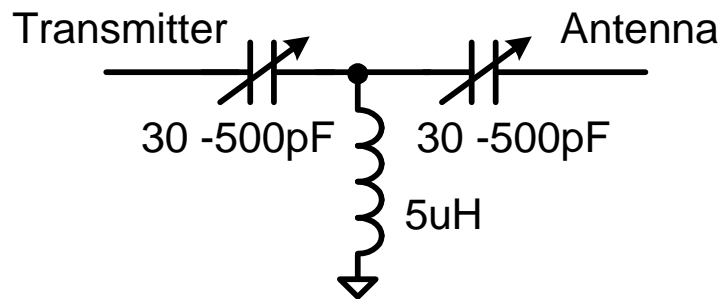- Fixed "L" can cover 2 bands pretty well.
- Inductor easy to make very high Q.
- Coupler best @ ~5MHz
- Matches all 10:1 SWRs & 95% of 20:1 SWRs





High Pass "Tee" Network
"C-Fixed L-C"

5 MHz

Fixed "L" High Pass "Tee" Network

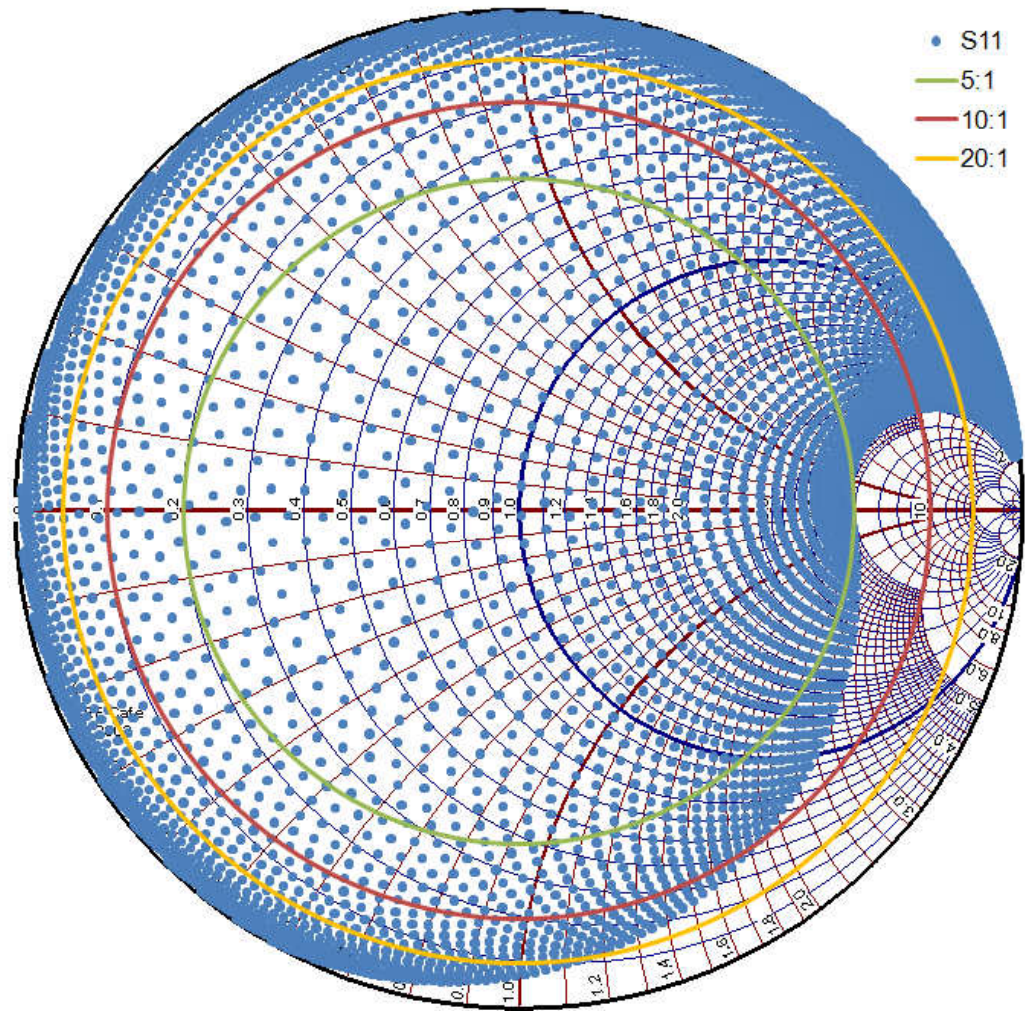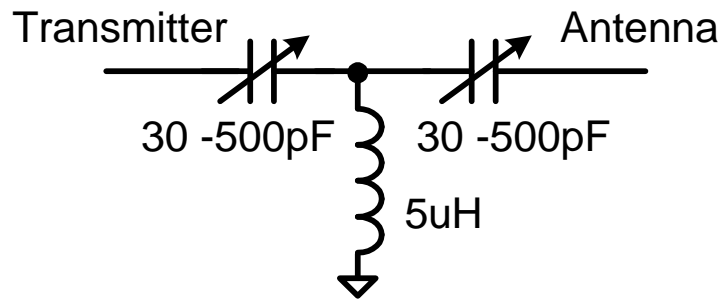- Matches all 5:1 SWRs & 75% of 20:1 SWRs





High Pass "Tee" Network
"C-Fixed L-C"

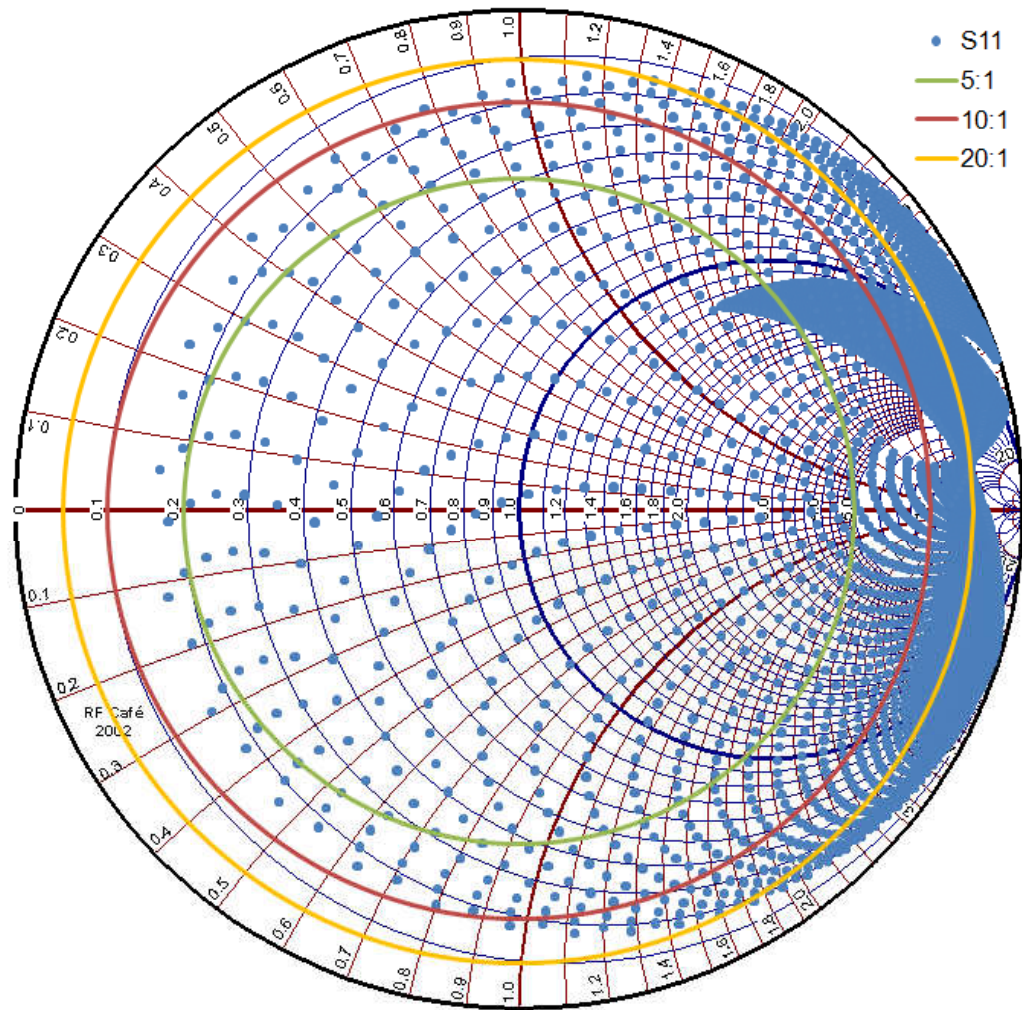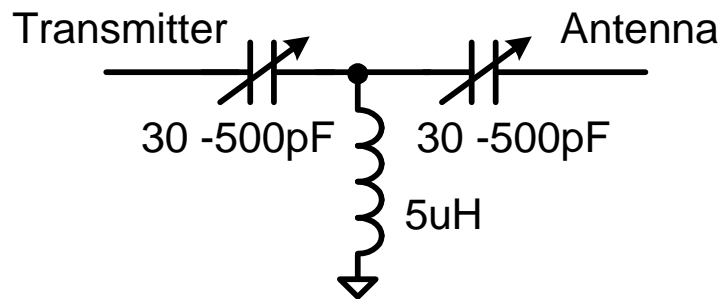3.5 MHz

Fixed "L" High Pass "Tee" Network

- Matches all 7:1 SWRs, 60% of 10:1 SWRs, & 40% of 20:1 SWRs




High Pass "Tee" Network
"C-Fixed L-C"


7 MHz

Other Network Topologies

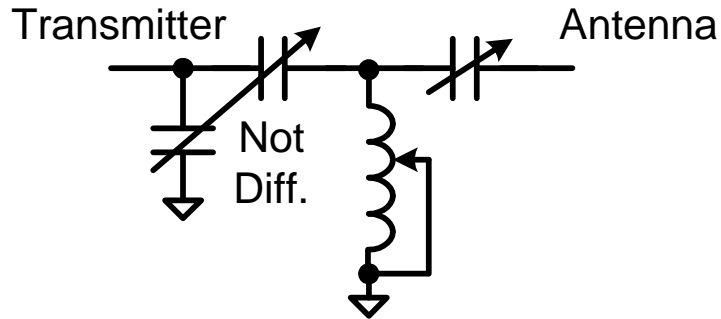- Lew McCoy W1ICP, Ultimate Transmatch (1970)




- Doug DeMaw W1FB, SPC Transmatch (1980)

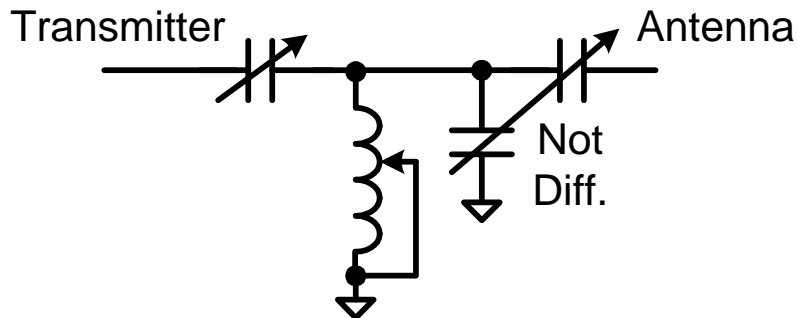

Both had minimal to moderate harmonic suppression with a reduction in matching range vs the basic High Pass “Tee”.

Other Network Topologies


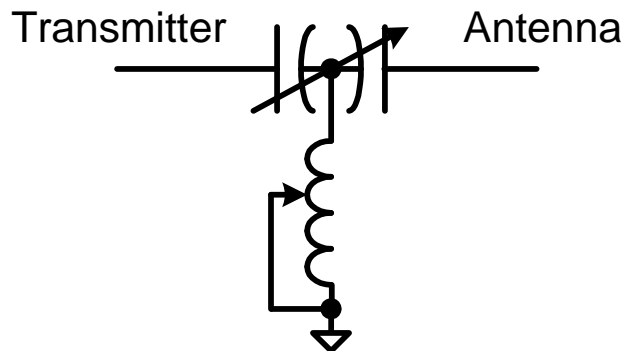
- Link Coupled (Johnson Matchbox)
 - Very good for higher R matches
 - Link coupling very efficient
- High Pass Differential Tee (MFJ & later Palstar)
 - Only 2 controls to adjust



Slightly to significantly more loss than standard High Pass Tee & reduced matching range on higher frequencies but easier to adjust.

High Pass Differential "Tee" Network

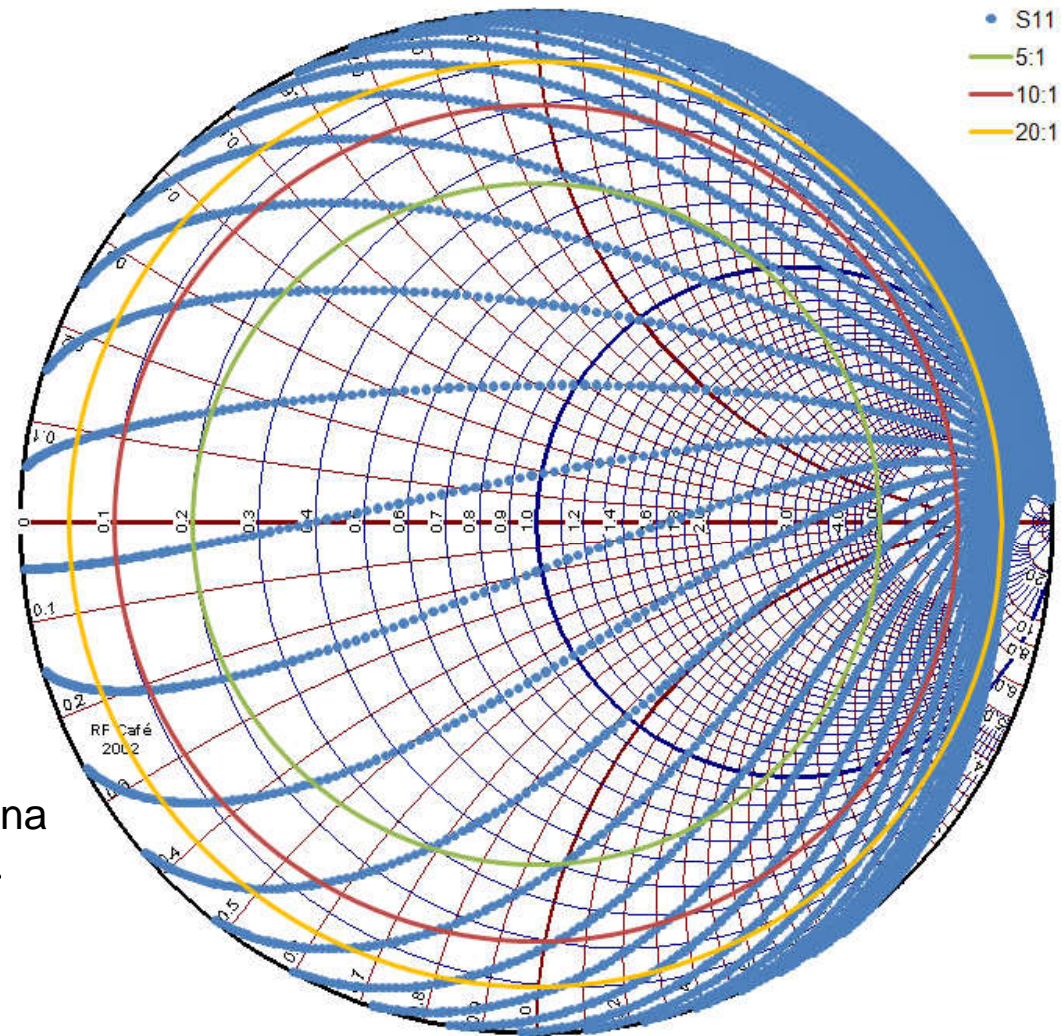
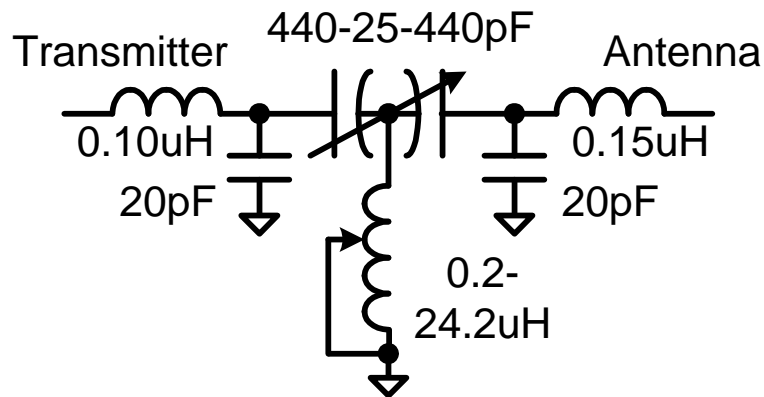
- Based on measurements and component values of the Palstar AT-Auto with last version of inductor



High Pass Differential "Tee" C-L-C 1.8 MHz

High Pass Differential "Tee" Network



– Palstar AT-Auto

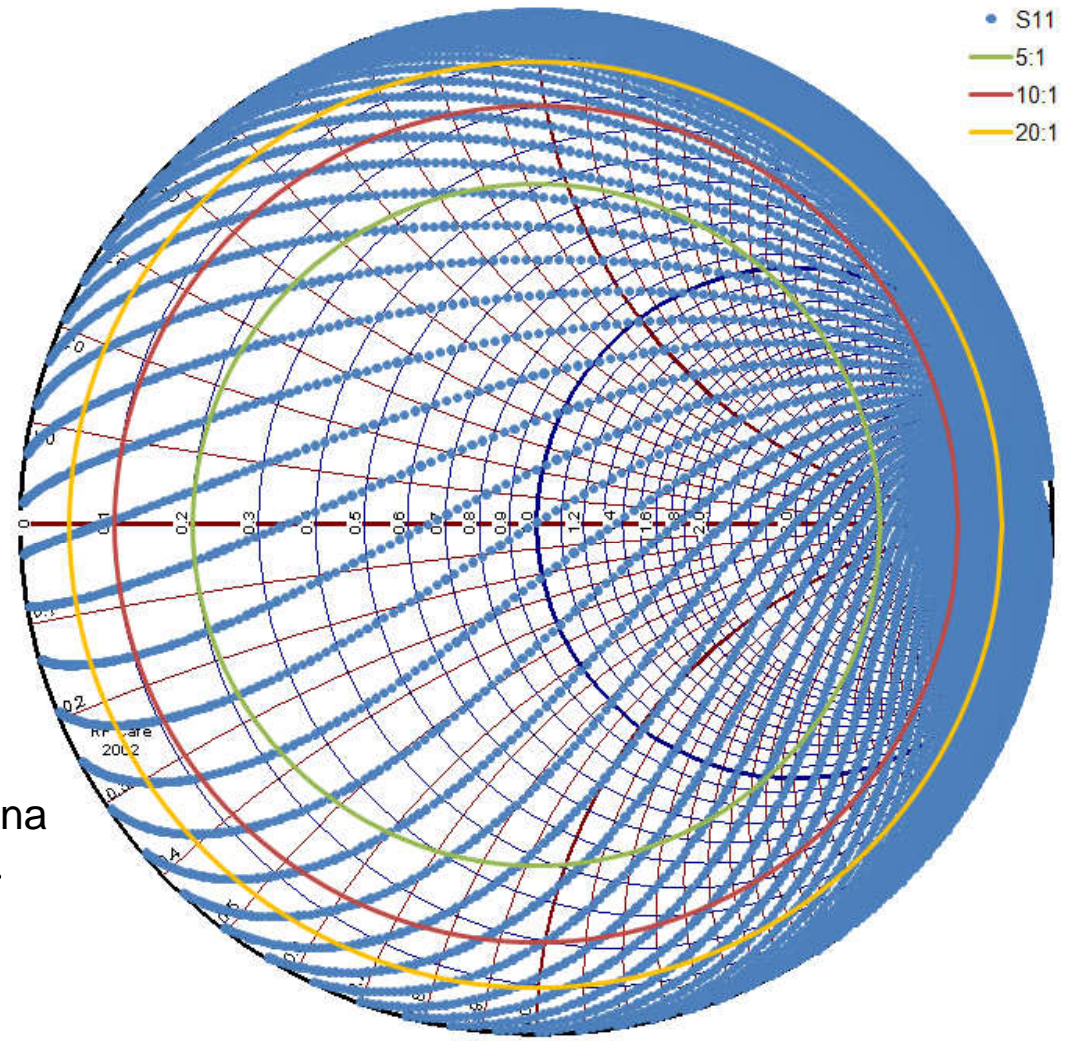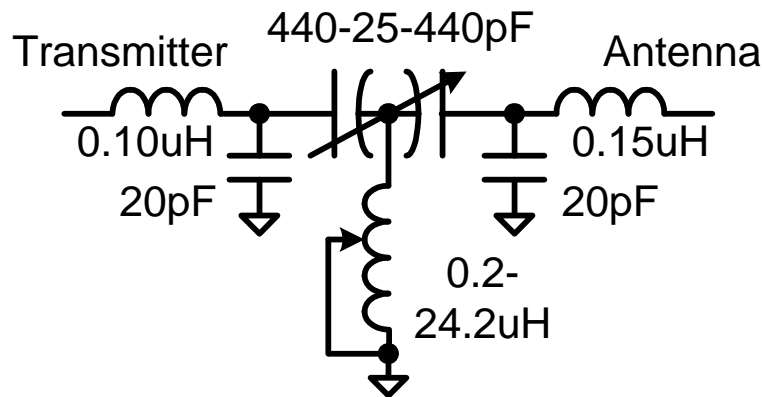

High Pass Differential "Tee" C-L-C 3.5 MHz

High Pass Differential "Tee" Network



– Palstar AT-Auto

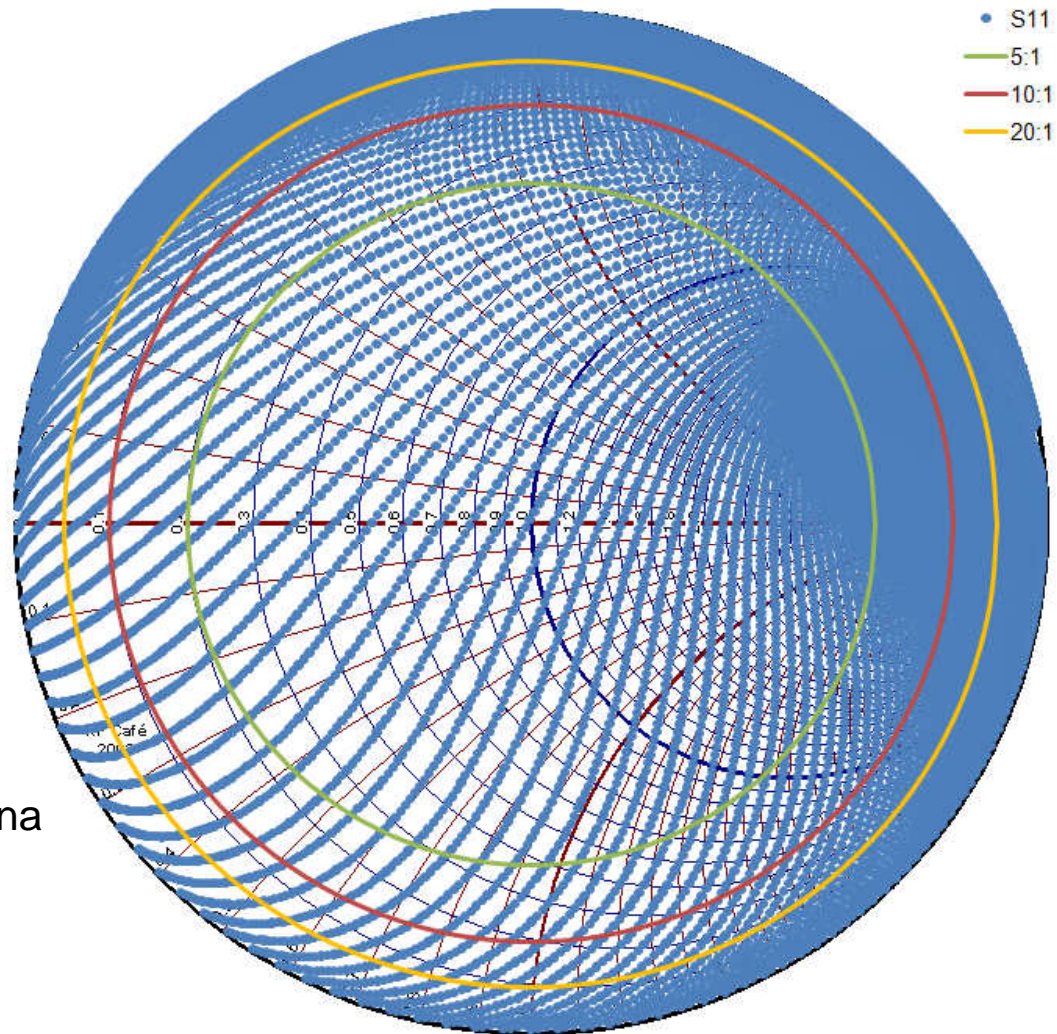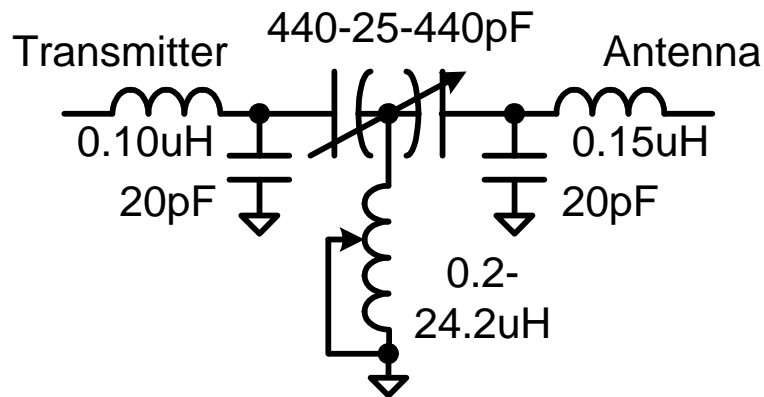

High Pass Differential "Tee" C-L-C 7 MHz

High Pass Differential "Tee" Network

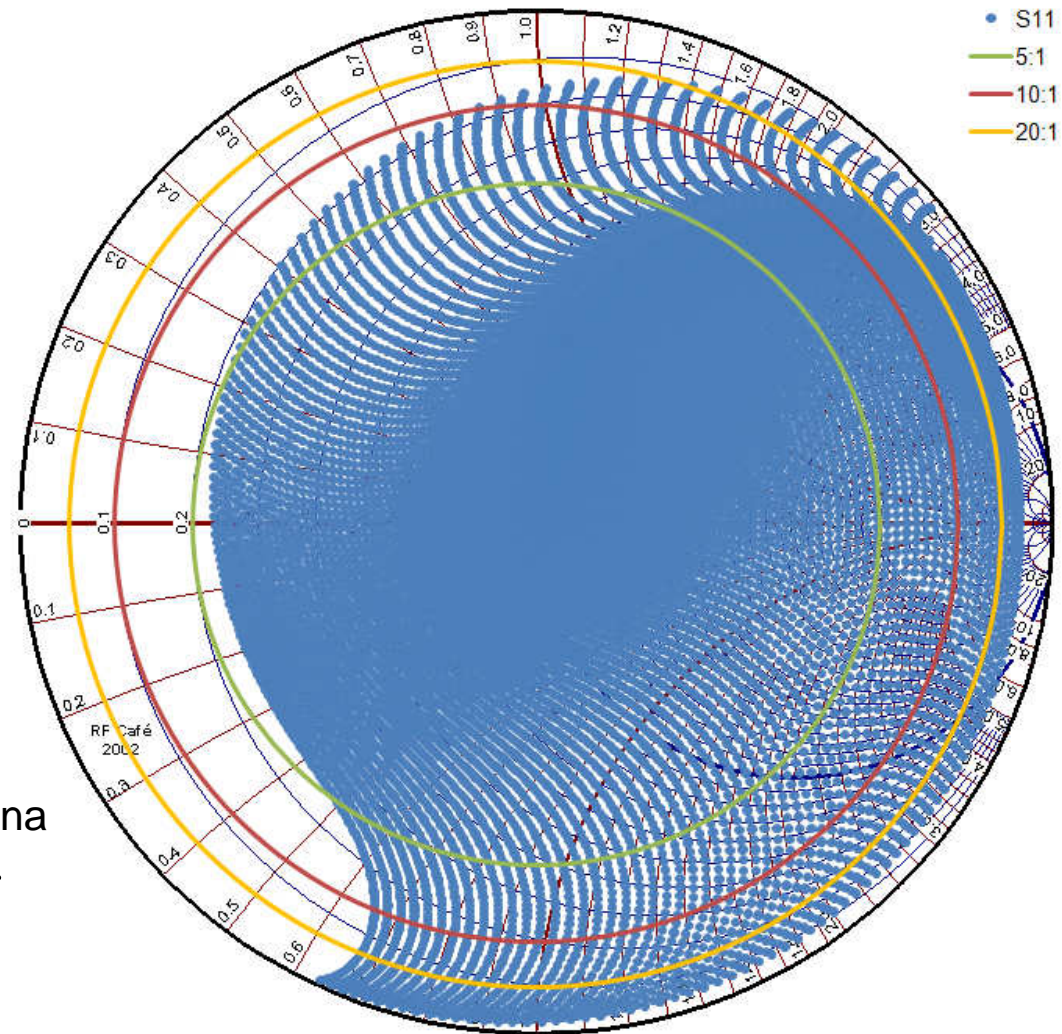
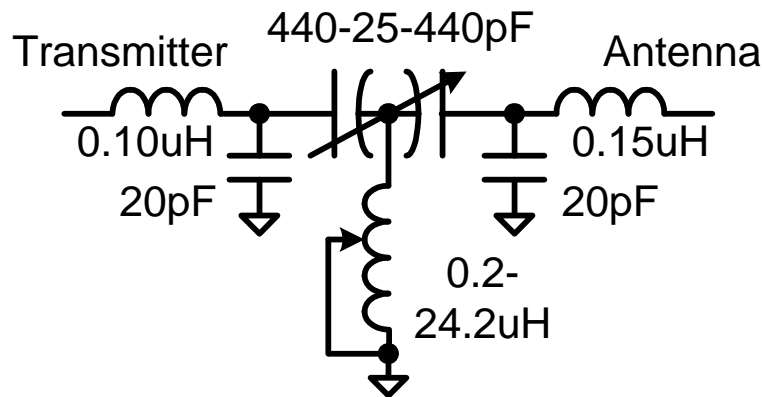
- Palstar AT-Auto
- No longer matches all 5:1 SWRs
- Add 4' of 50Ω .66VF coax for 90 deg. CW rotation if needed.



High Pass Differential "Tee" C-L-C 21 MHz

High Pass Differential "Tee" Network

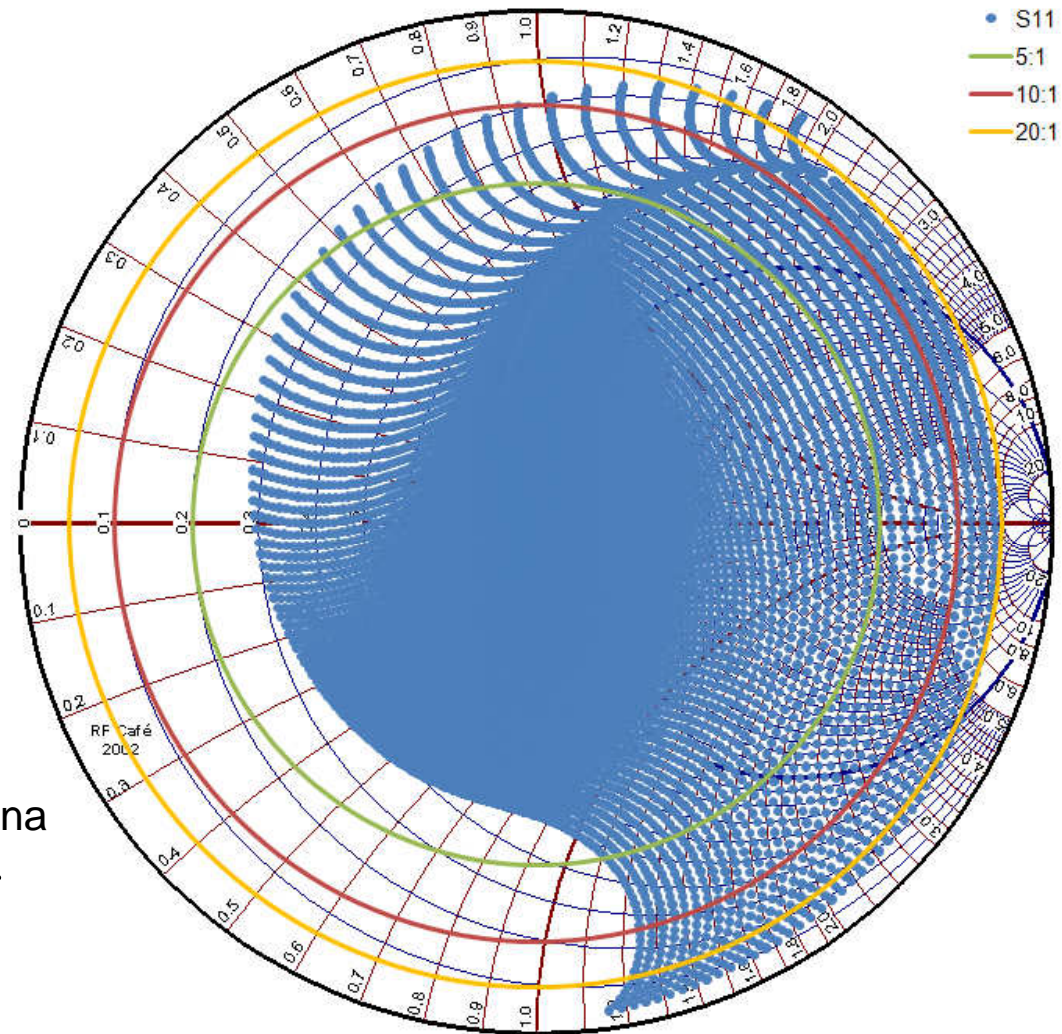
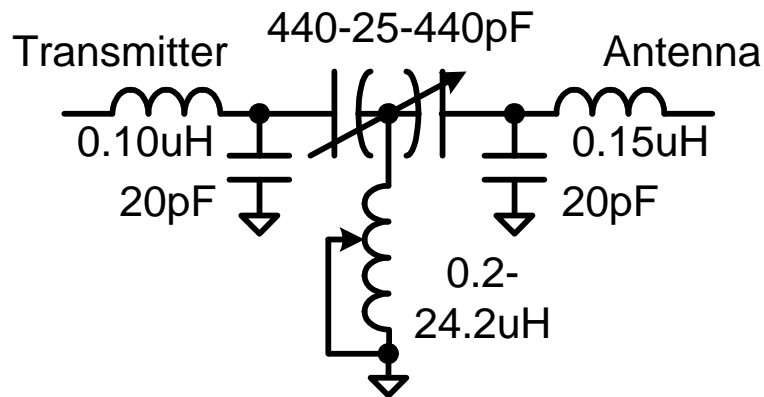
- Palstar AT-Auto
- Matching range severely reduced



High Pass Differential "Tee" C-L-C 28 MHz

High Pass Differential "Tee" Network

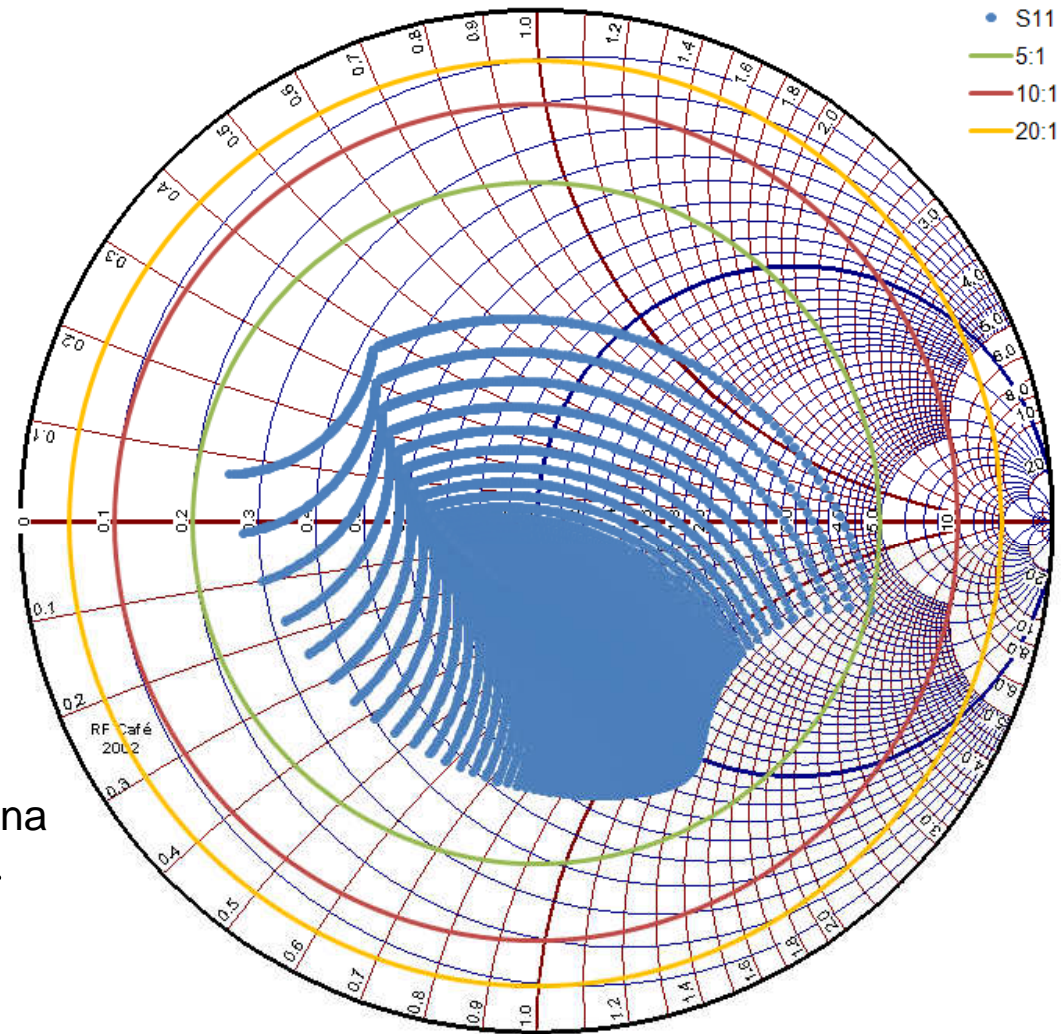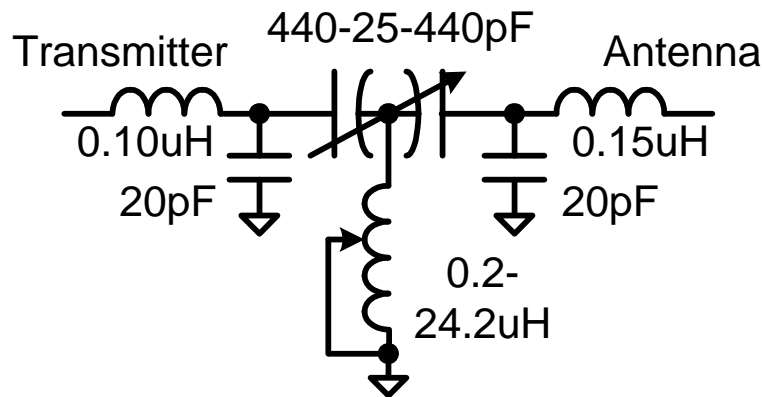- Palstar AT-Auto
- Matching range very limited



High Pass Differential "Tee" C-L-C 54 MHz

The End!

Other Topics

- Why might a full sized dipole need matching?
- Coupler topologies and stresses.
- Converting series to parallel impedances.
- Johnson Matchbox or other link couplers.
- Quarter wave section for variable impedances.
- Transmission line only tuner.
- Complex conjugate impedances.
- Graphical look at reflections.

Does a Full Sized Dipole Need Matching?

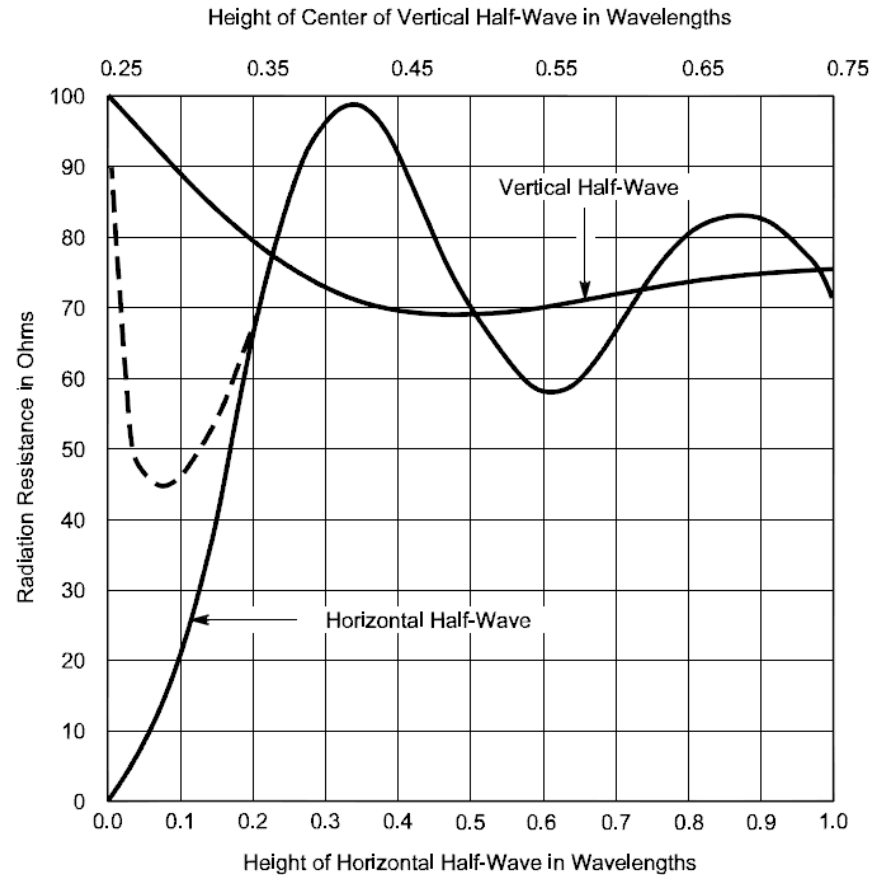
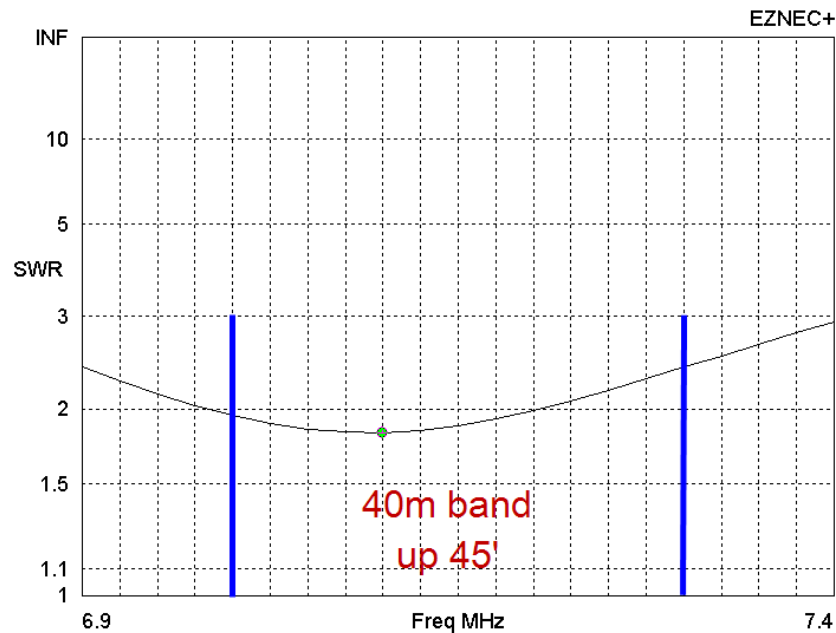


Fig 1—Variation in radiation resistance of vertical and horizontal half-wave antennas at various heights above flat ground. Solid lines are for perfectly conducting ground; the broken line is the radiation resistance of horizontal half-wave antennas at low height over real ground. Chapter 3, ARRL Antenna Book 21st edition

Dipole Matching

- 7.0MHz = $88.9 - j13.8$ 7.1MHz = $93.2 + j8.1$
7.2MHz = $97.7 + j29.9$ 7.3MHz = $102.2 + j51.5$
- Match with 99 deg. of 75Ω transmission line at antenna. SWR < 1.4:1 across entire band.
- Match with 2.55uH across antenna and 408pF in series toward TX. SWR < 1.4:1 across entire band.
- All matches with Q significantly less than the Q of the dipole will have 1.4:1 band edge SWRs.

$Z = 20 - j0$ (SWR 2.5:1), 28MHz, 1500W

Type	Transmitter Side		Antenna Side
LP-"L" Cp-Ls	Cp = 139.2pF 387Vpk, 6.7A	Ls = 0.14uH 300Vpk, 8.7A	
HP-"L" Lp-Cs	Lp = 0.23uH 387Vpk, 6.7A	Cs = 232pF 300Vpk, 8.7A	
HP-"Tee" 250pF Cs1-Lp-Cs2	Cs1 = 250pF 176Vpk, 5.5A	Lp = 0.18uH 426Vpk, 9.4A	Cs2 = 200pF 348Vpk, 8.7A
HP-"Tee" 500pF Cs1-Lp-Cs2	Cs1 = 500pF 88Vpk, 5.5A	Lp = 0.20uH 397Vpk, 8.0A	Cs2 = 223pF 313Vpk, 8.7A
LP-"Pi" 200pF Cp1-Ls-Cp2	Cp1 = 188.1pF 387Vpk, 9.1A	Ls = 0.18uH 472Vpk, 10.6A	Cp = 200pF 245Vpk, 6.1A

$Z = 5 - j200$ (SWR 157:1), 1.8MHz, 1500W

Type	Transmitter Side		Antenna Side
LP-"L" Cp-Ls	Cp = 5302pF 387Vpk, 16.4A	Ls = 19.01uH 5265Vpk, 17.3A	
HP-"L" Cs-Lp	Cs = 140.3pF 4882Vpk, 5.5A	Lp = 13.45uH 4897Vpk, 22.8A	
HP-"Tee" 250pF Cs1-Lp-Cs2	Cs1 = 50.7pF 13511Vpk, 5.5A	Lp = 37.17uH 13517Vpk, 22.7A	Cs2 = 250pF 8634Vpk, 17.3A
HP-"Tee" 500pF Cs1-Lp-Cs2	Cs1 = 74.4pF 9205Vpk, 5.5A	Lp = 25.31uH 9213Vpk, 22.8A	Cs2 = 500pF 4323Vpk, 17.3A
HP-"Tee" 1000pF Cs1-Lp-Cs2	Cs1 = 97.2pF 7046Vpk, 5.5A	Lp = 19.38uH 7056Vpk, 22.8A	Cs2 = 1000pF 2163Vpk, 17.3A
LP-"Pi" 100pF Cp1-Ls-Cp2	Cp1 = 6621pF 387Vpk, 20.5A	Ls = 15.53uH 5270Vpk, 21.2A	Cp = 100pF 4897Vpk, 3.9A
LP-"Pi" 1000pF Cp1-Ls-Cp2	Cp1 = 18103pF 387Vpk, 56.1A	Ls = 5.85uH 5270Vpk, 56.3A	Cp = 1000pF 4884Vpk, 39.1A

$Z = 2000 - j0$ (SWR 40:1), 7.0MHz, 1500W

Type	Transmitter Side		Antenna Side
LP-"L" Ls-Cp	Ls = 7.10uH 2148Vpk, 5.5A	Cp = 71.0pF 2449Vpk, 5.4A	
HP-"L" Cs-Lp	Cs = 72.8pF 2418Vpk, 5.5A	Lp = 7.28uH 2449Vpk, 5.4A	
HP-"Tee" 250pF Cs1-Lp-Cs2	Cs1 = 72.7pF 2421Vpk, 5.5A	Lp = 7.23uH 2452Vpk, 5.4A	Cs2 = 250pF 111Vpk, 0.9A
HP-"Tee" 500pF Cs1-Lp-Cs2	Cs1 = 72.8pF 2419Vpk, 5.5A	Lp = 7.25uH 2450Vpk, 5.4A	Cs2 = 500pF 56Vpk, 0.9A
LP-"Pi" 250pF Cp1-Ls-Cp2	Cp1 = 250pF 387Vpk, 3.0A	Ls = 6.74uH 2610Vpk, 6.2A	Cp = 81pF 2449Vpk, 6.2A
LP-"L" Ls-Cp	Ls = 7.10uH 2148Vpk, 5.5A	Cp = 71.0pF 2449Vpk, 5.4A	

Series/Parallel Conversion

$$R_p = \frac{R_s^2 + X_s^2}{R_s}$$

$$X_p = \frac{R_s^2 + X_s^2}{X_s}$$

$$R_s = \frac{R_p \times X_p^2}{R_p^2 + X_p^2}$$


$$X_s = \frac{R_p^2 \times X_p}{R_p^2 + X_p^2}$$

Note: If impedance was capacitive in series form then it is still capacitive in parallel form. Same is true for inductive impedances. Sign of X_p and X_s is the same.

80m full size dipole

- #12 wire up 40'
- No feedline
- Pink dot = 1.8MHz

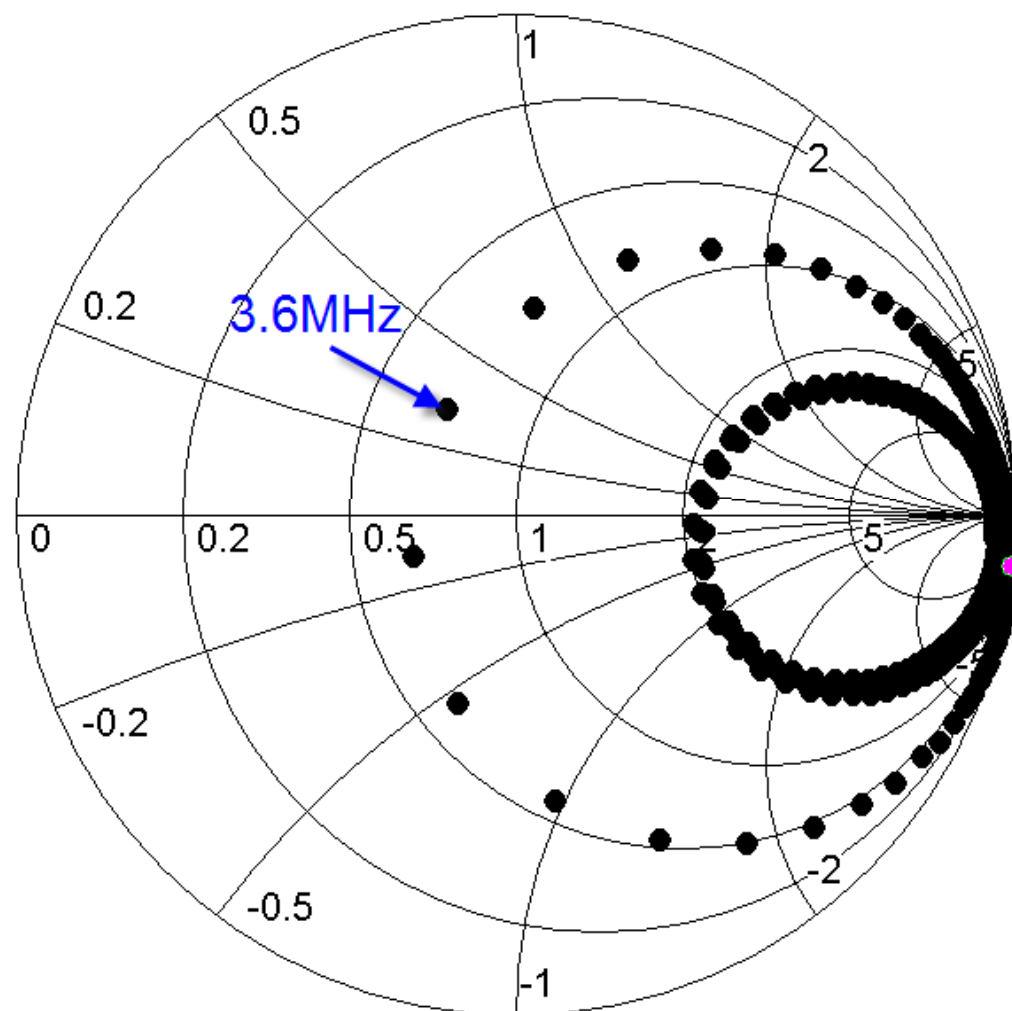What can be expected when used at all HF frequencies?




80m full size dipole

- 50' of .66VF 50Ω lossless coax

Very wide range of impedances!

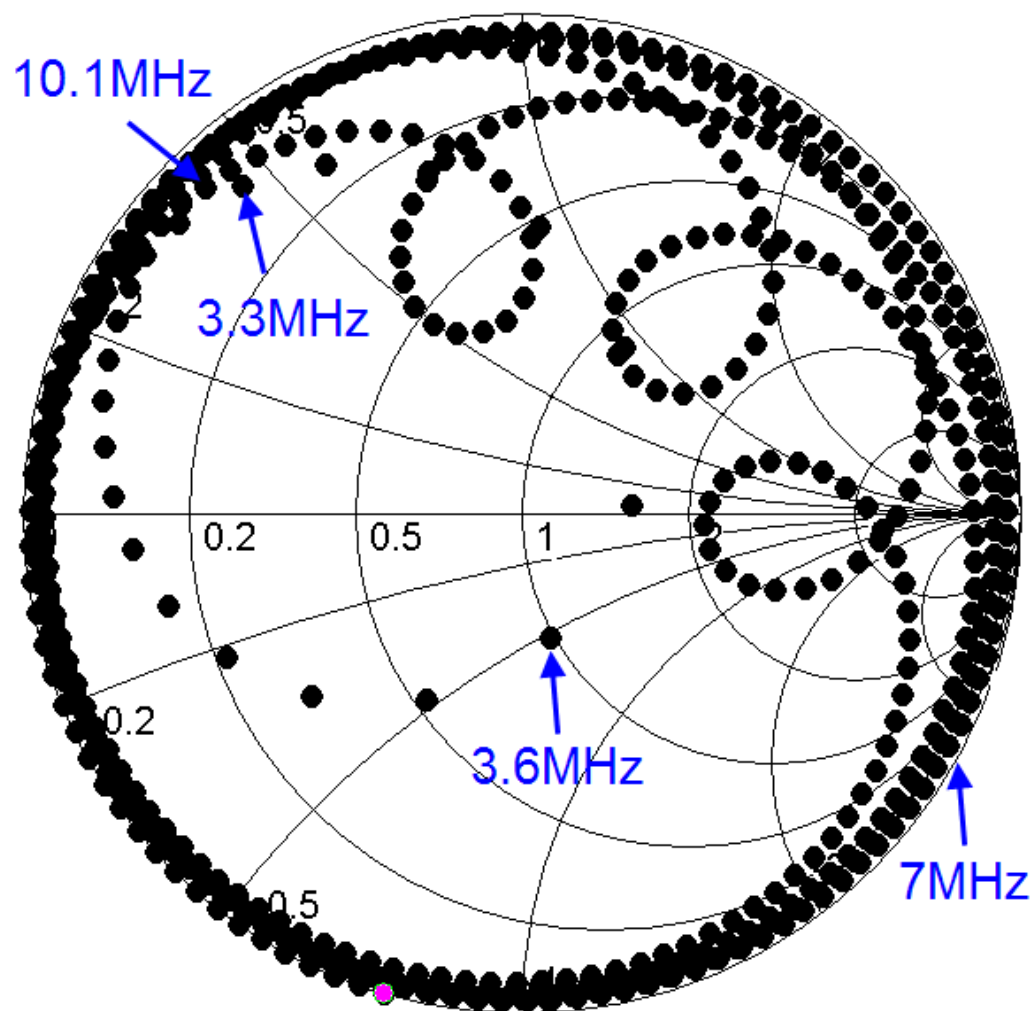Even if loss in real coax is ignored this is a tough matching problem.




80m full size dipole

- 50' of 600Ω lossless open wire line



Notice how impedances are high at all freq. above 3.5MHz.

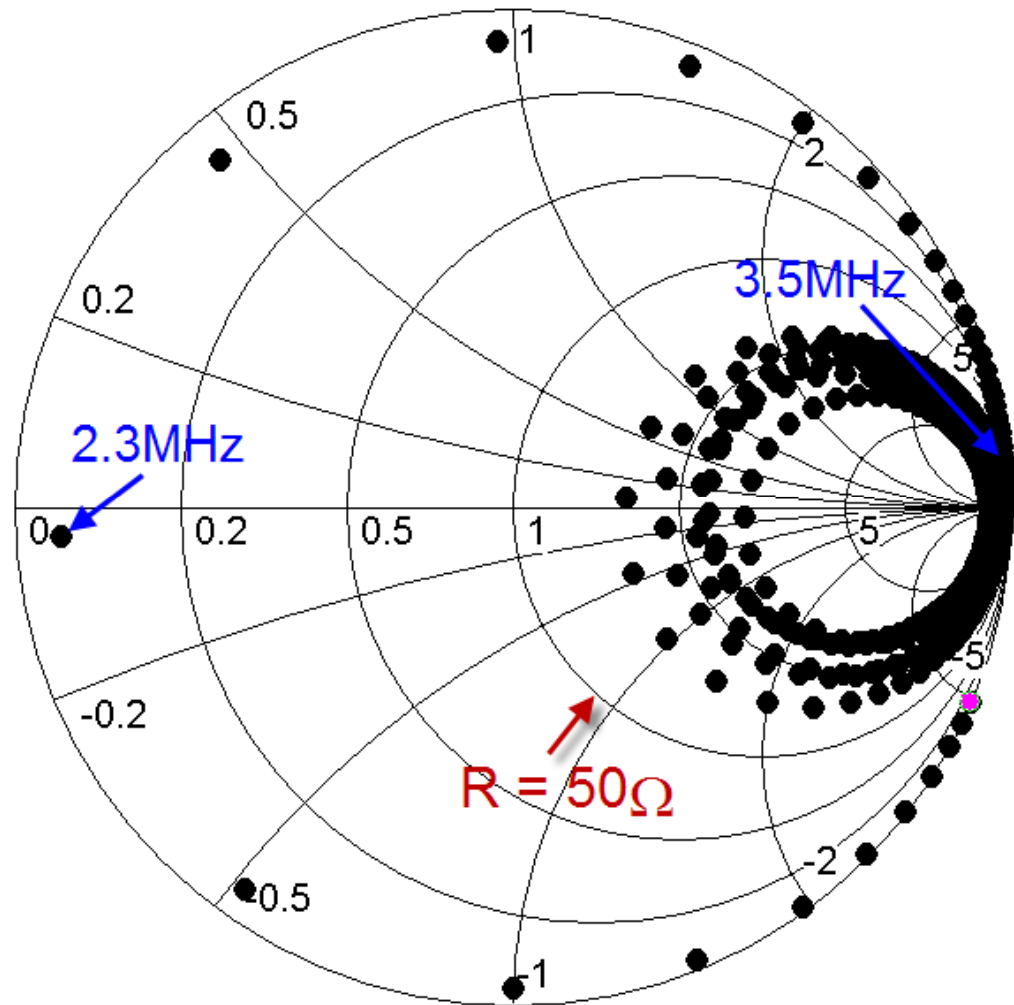The Johnson Matchbox efficiently matches higher impedances!





Lossless Transmission Line Reflections

1 electrical wavelength @ 14MHz

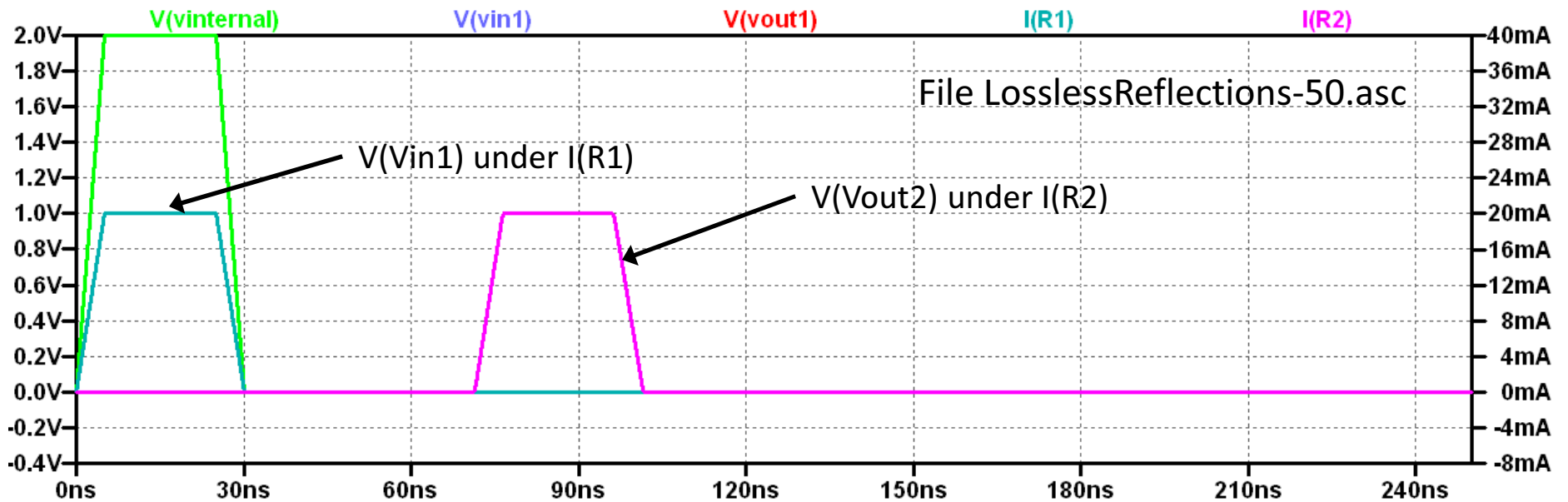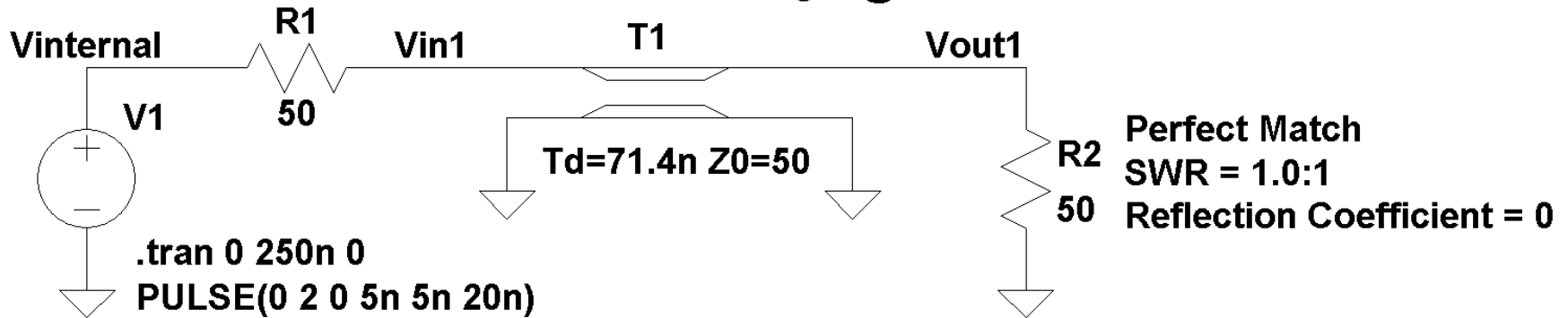


Lossless Transmission Line Reflections

1 electrical wavelength @ 14MHz

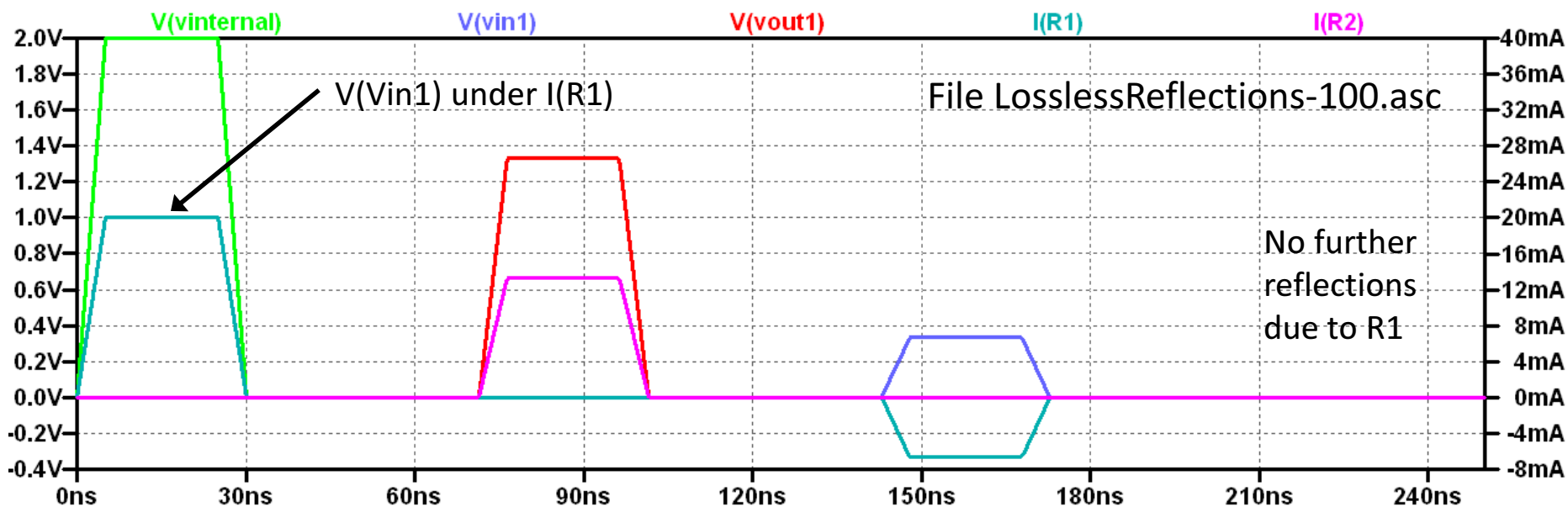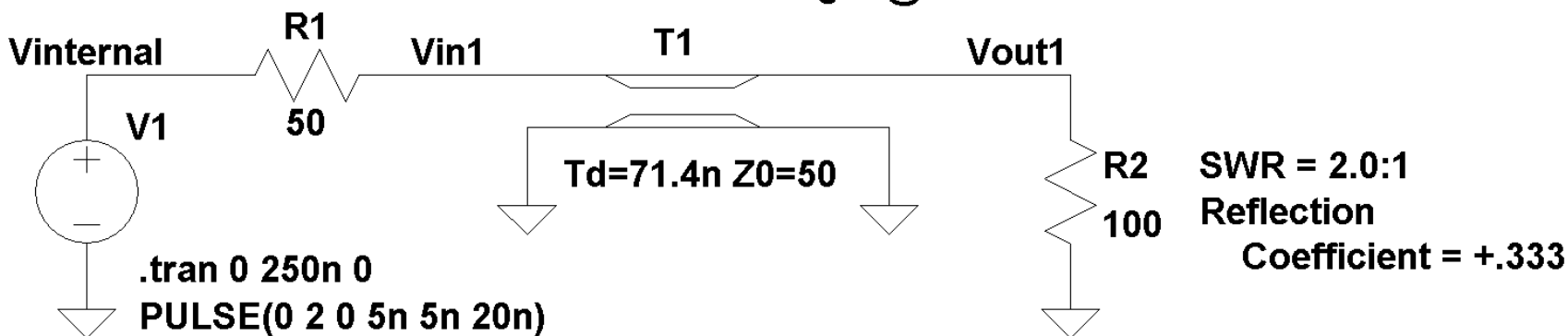


Lossless Transmission Line Reflections

1 electrical wavelength @ 14MHz

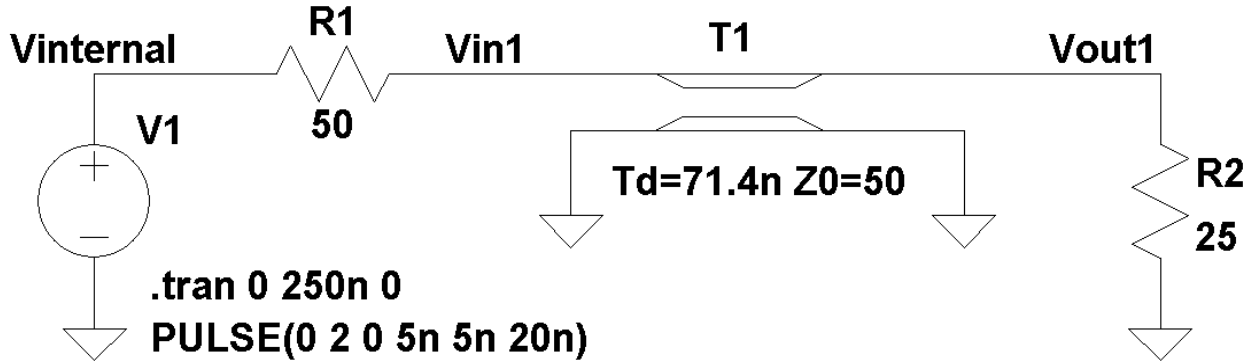


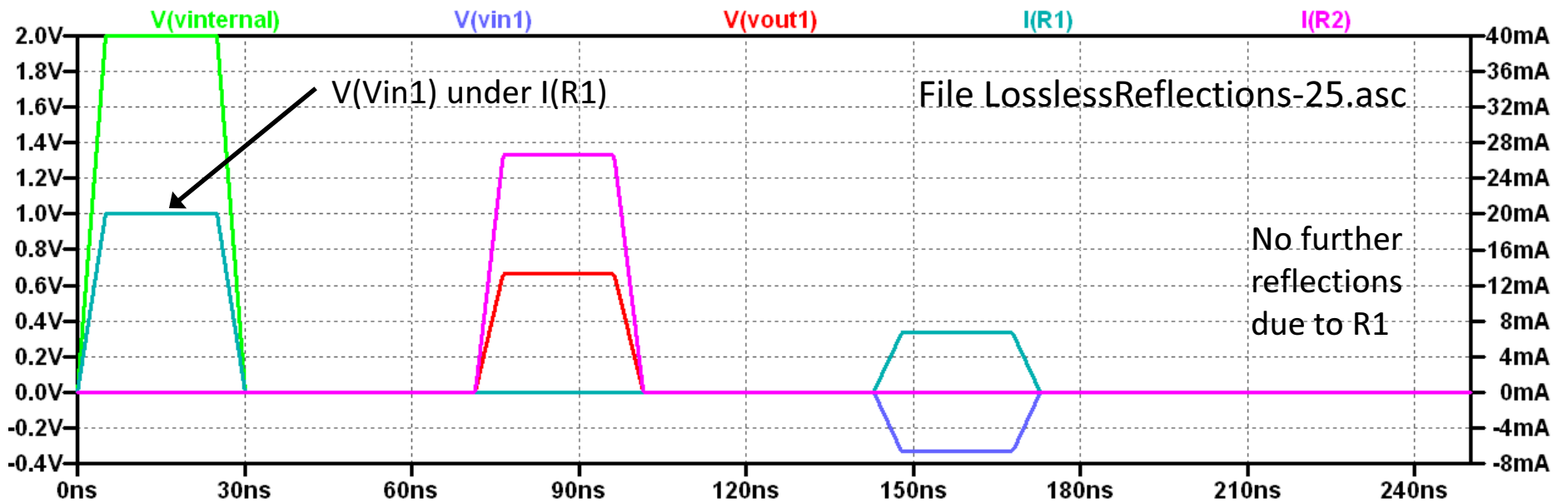SWR = 2.0:1
Reflection
Coefficient = -.333




Smith Chart

- Smith Chart basics
 - Z_0 at center, constant SWR = circles
 - X axis is reflection coefficient (-1 to +1)
 - Top half is inductive, bottom half is capacitive
 - Need to think in terms of $Z = R \pm jX$ & $Y = G \pm jB$
- The Smith Chart allows the user to see graphical solutions to matching problems which enhances the understanding of impedance matching
- Smith Chart could easily be an entire presentation

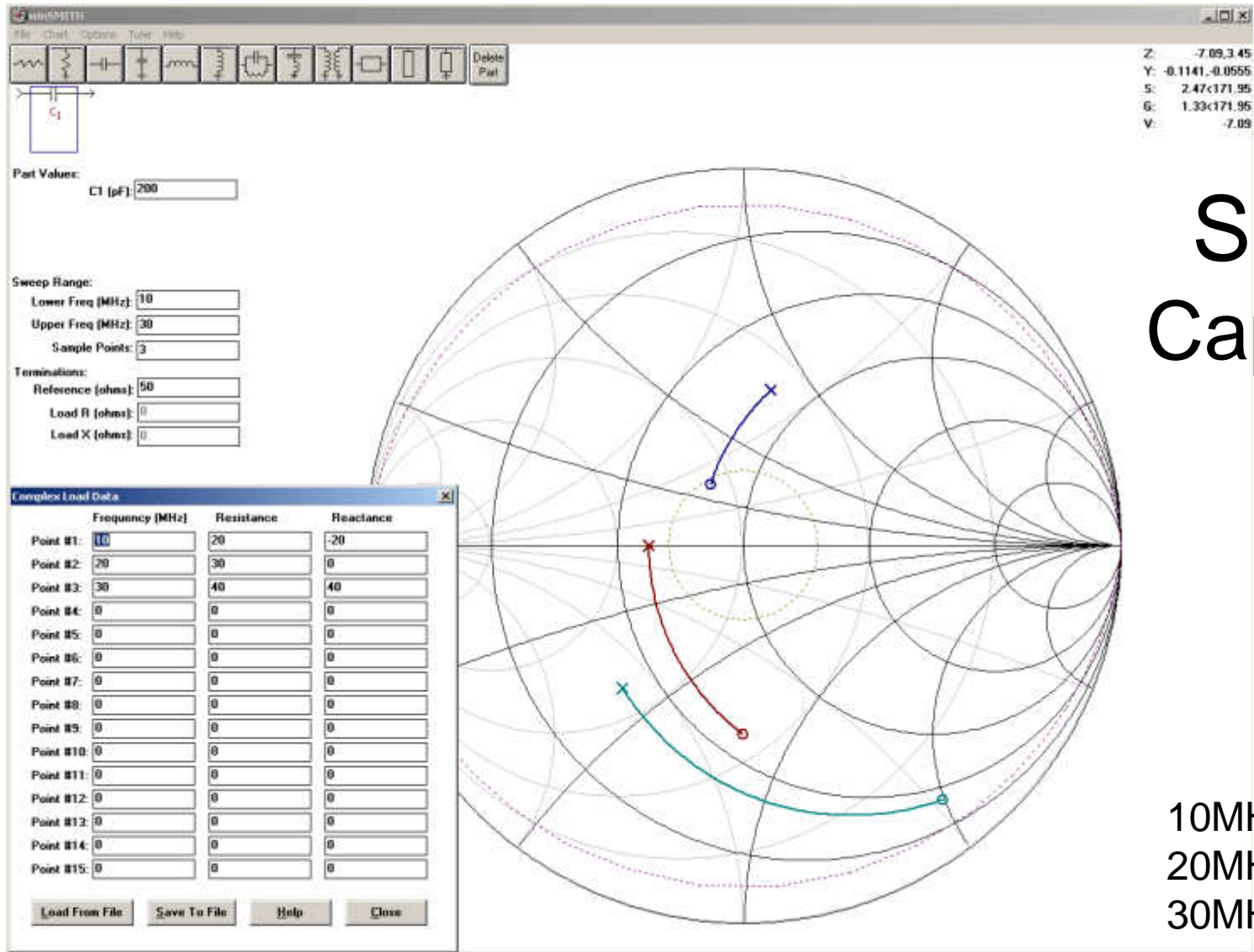


Series Capacitor

10MHz = Green
 20MHz = Red
 30MHz = Blue

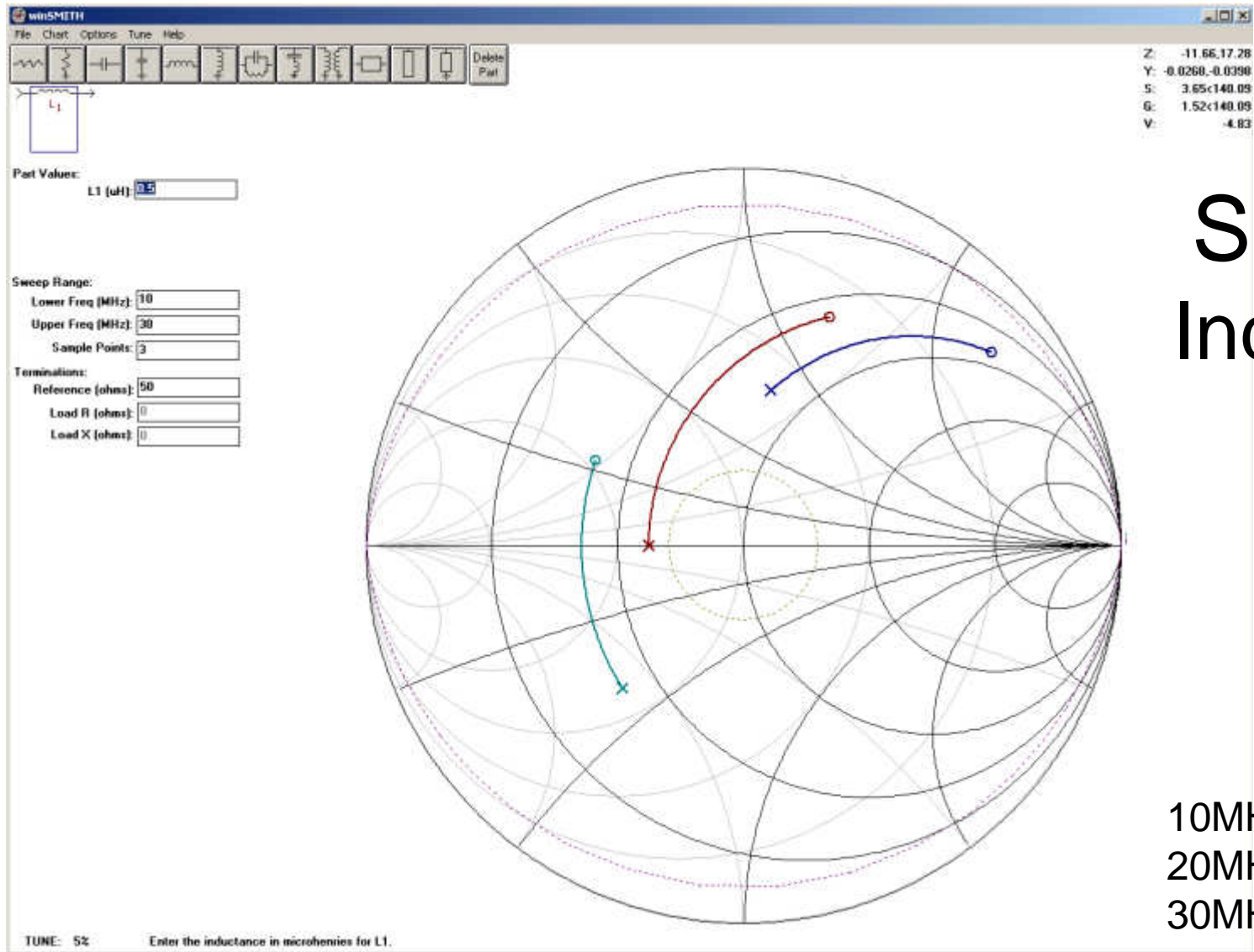


Series Inductor

10MHz = Green
20MHz = Red
30MHz = Blue

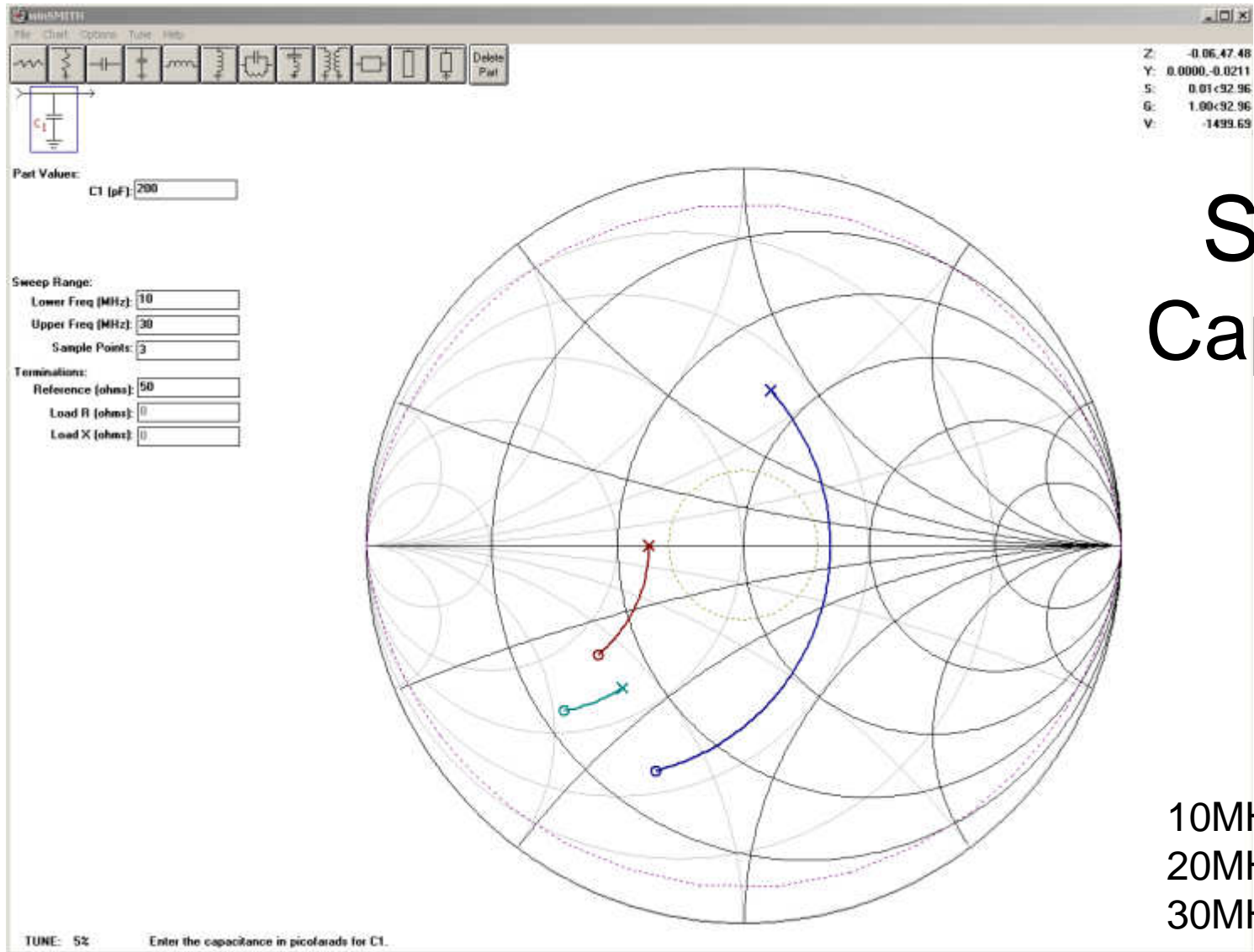


Shunt Capacitor

10MHz = Green
 20MHz = Red
 30MHz = Blue

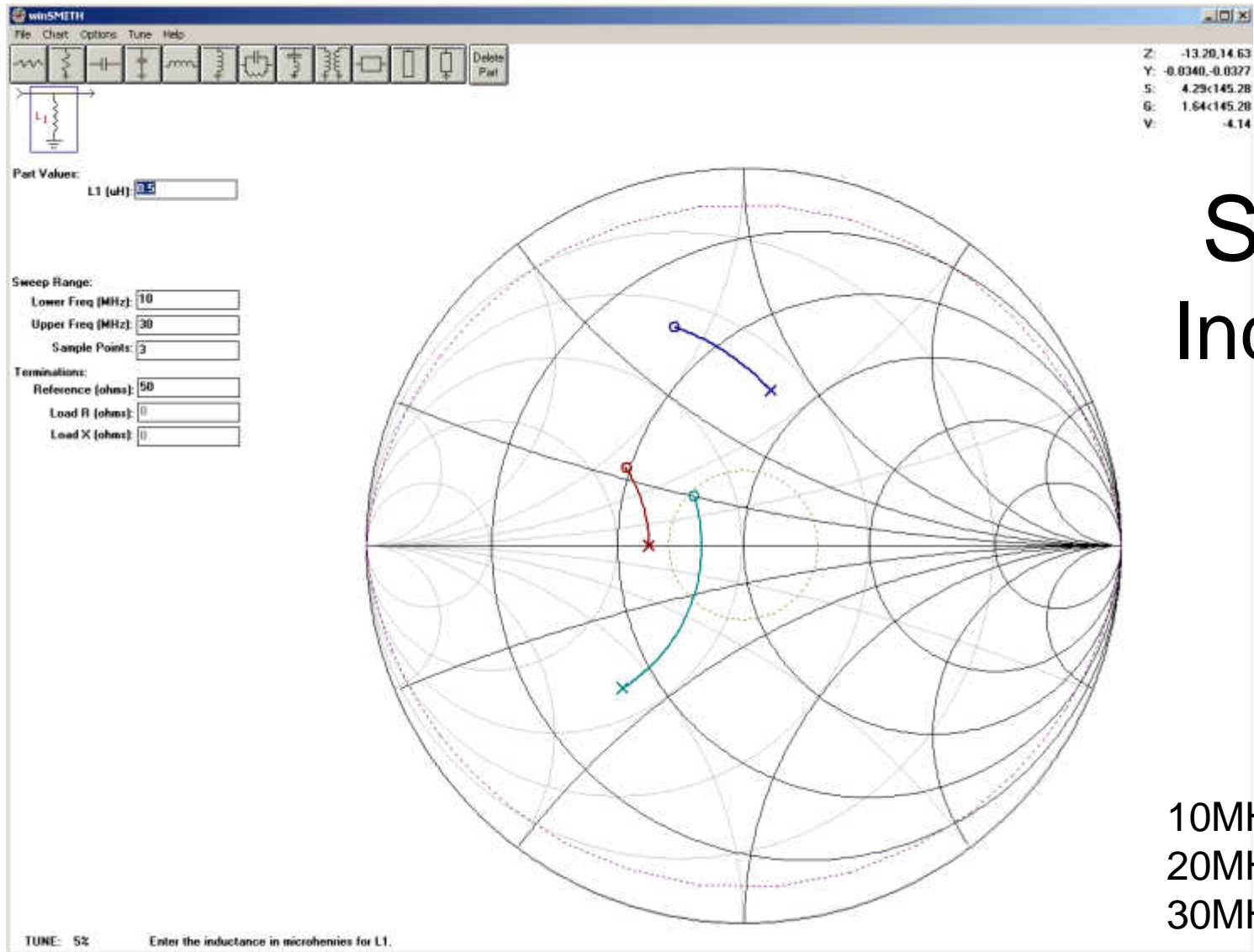


Shunt Inductor

10MHz = Green
 20MHz = Red
 30MHz = Blue

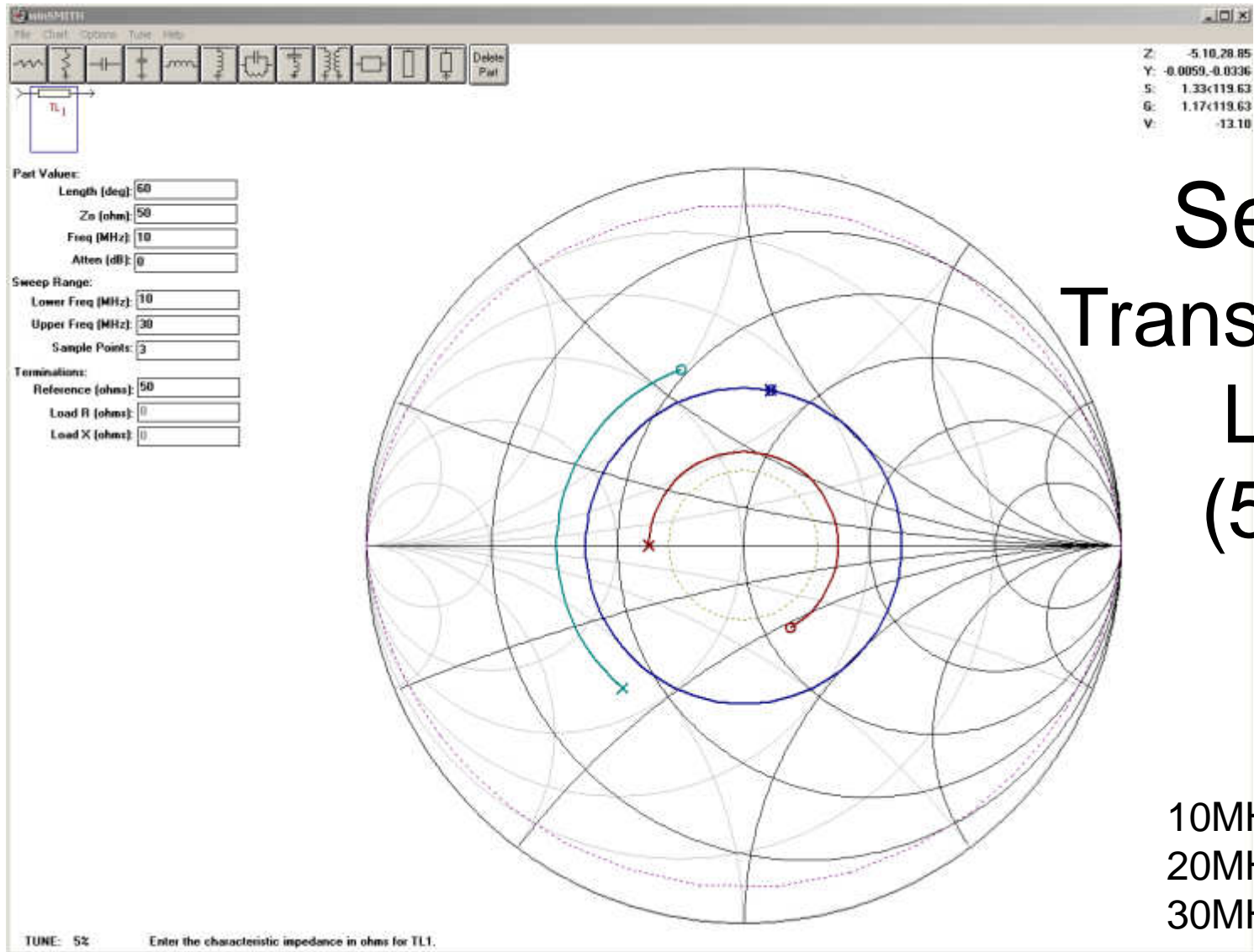


Series Transmission Line (50Ω)

10MHz = Green
 20MHz = Red
 30MHz = Blue

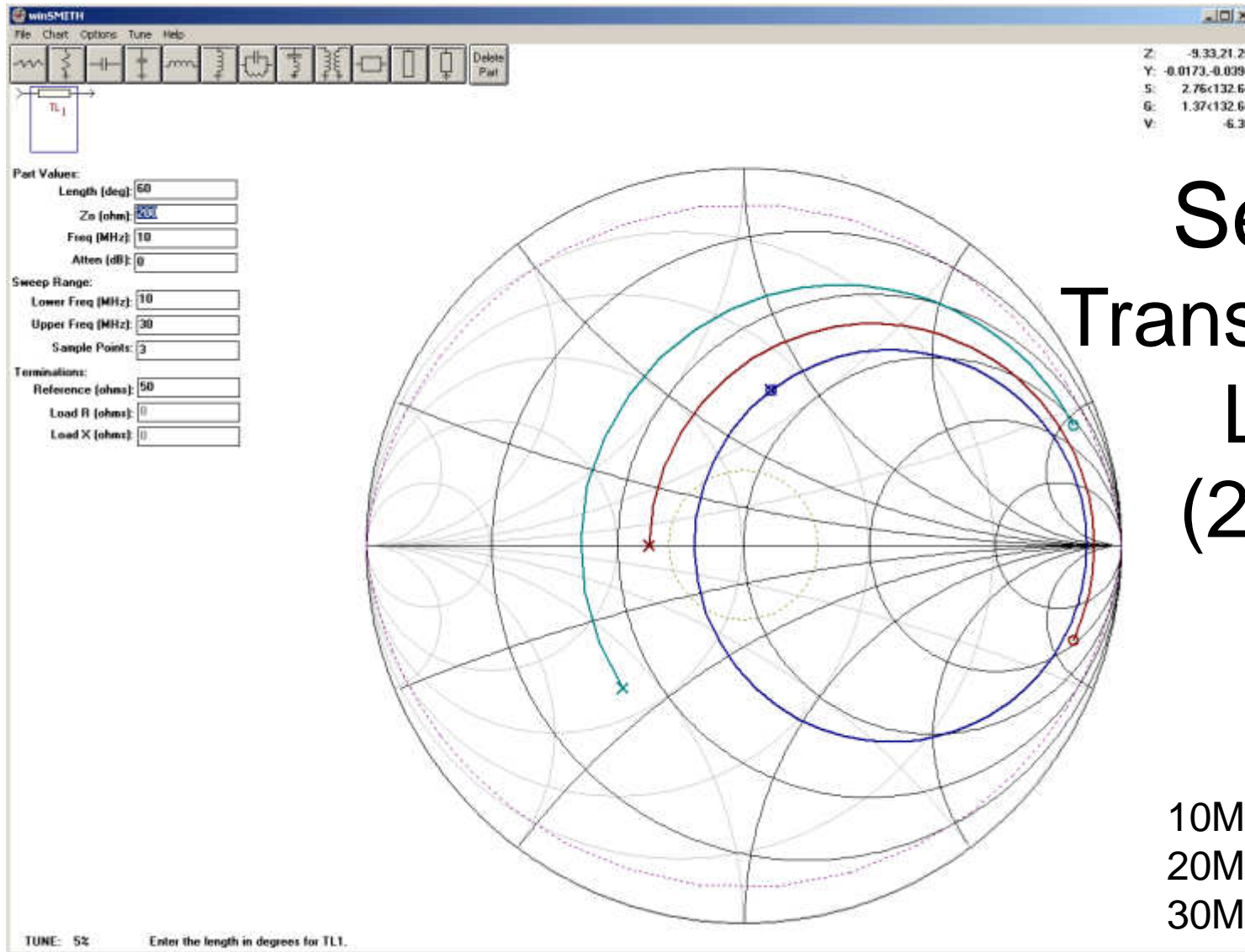


Series Transmission Line (200Ω)

10MHz = Green
20MHz = Red
30MHz = Blue

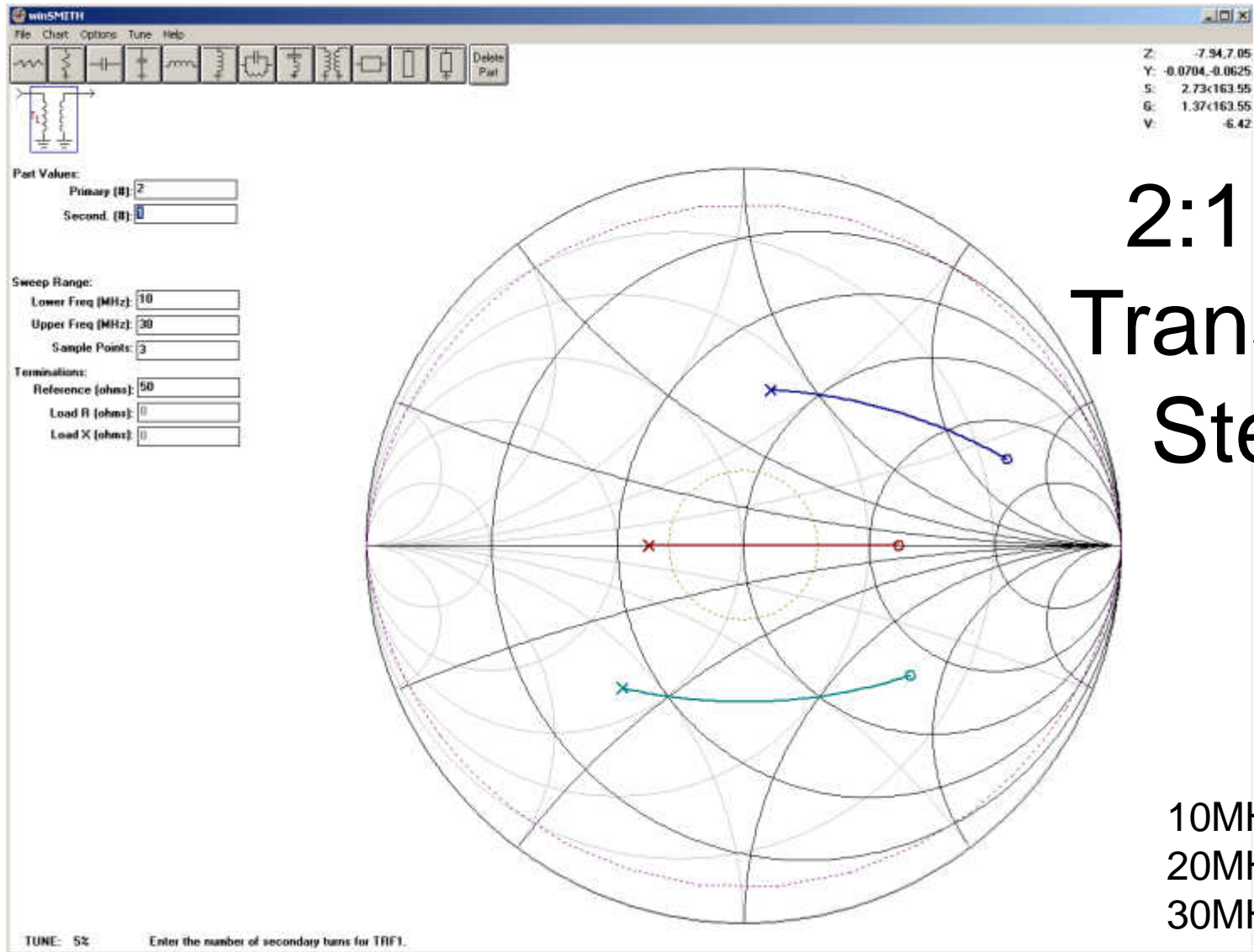


2:1 Turns Transformer Step Up

10MHz = Green
 20MHz = Red
 30MHz = Blue

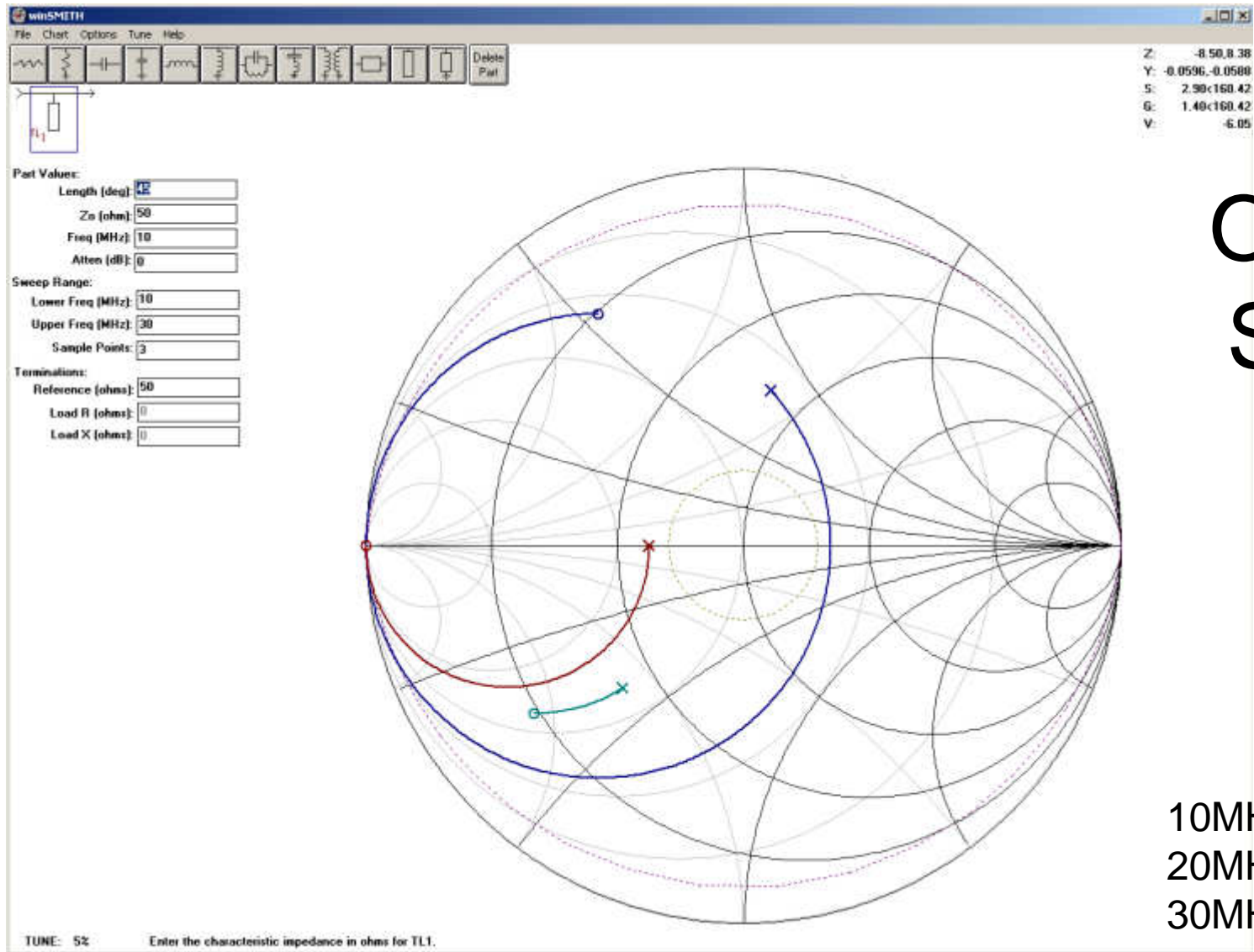


Open Stub

10MHz = Green
 20MHz = Red
 30MHz = Blue

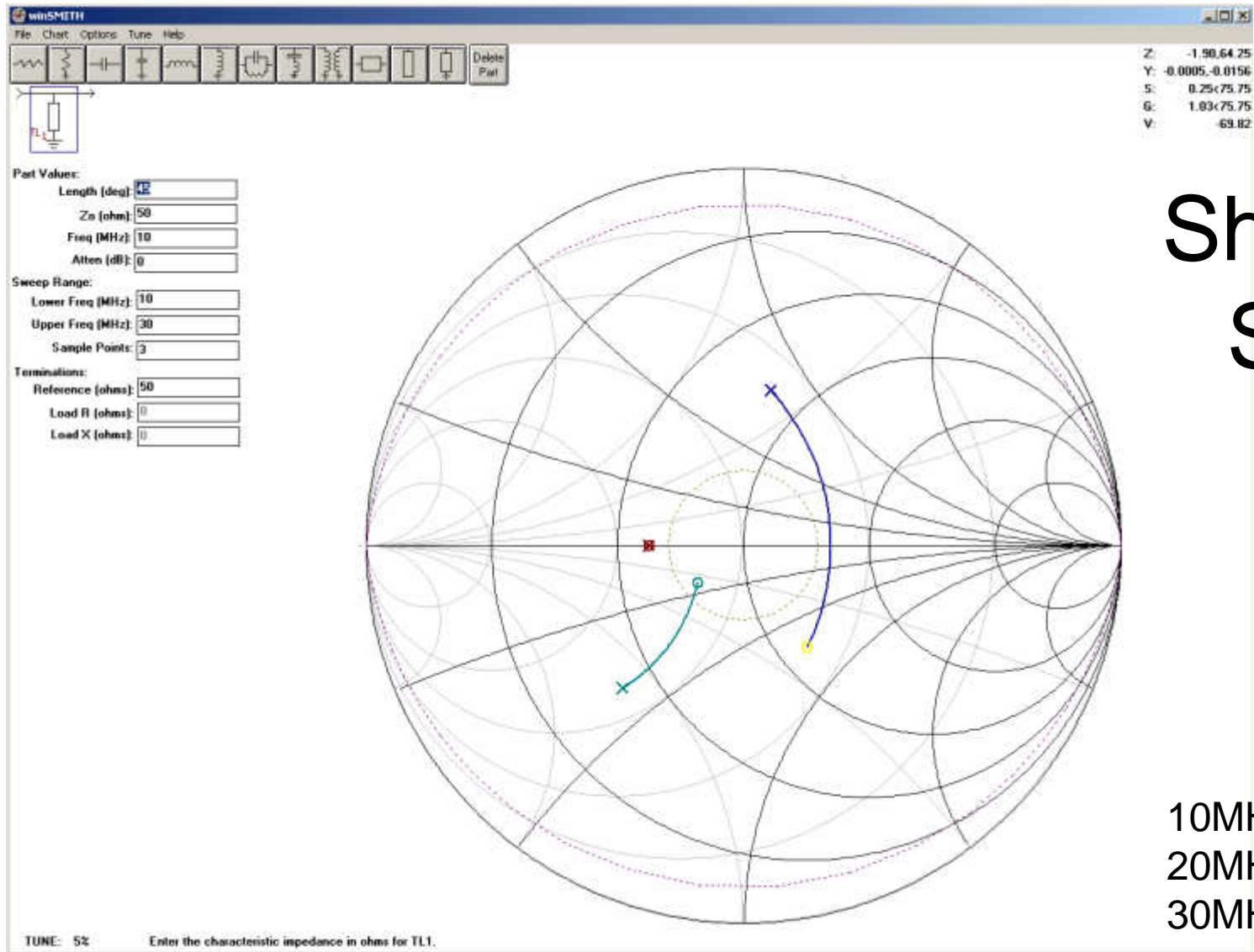


Shorted Stub

Smith Chart Regions

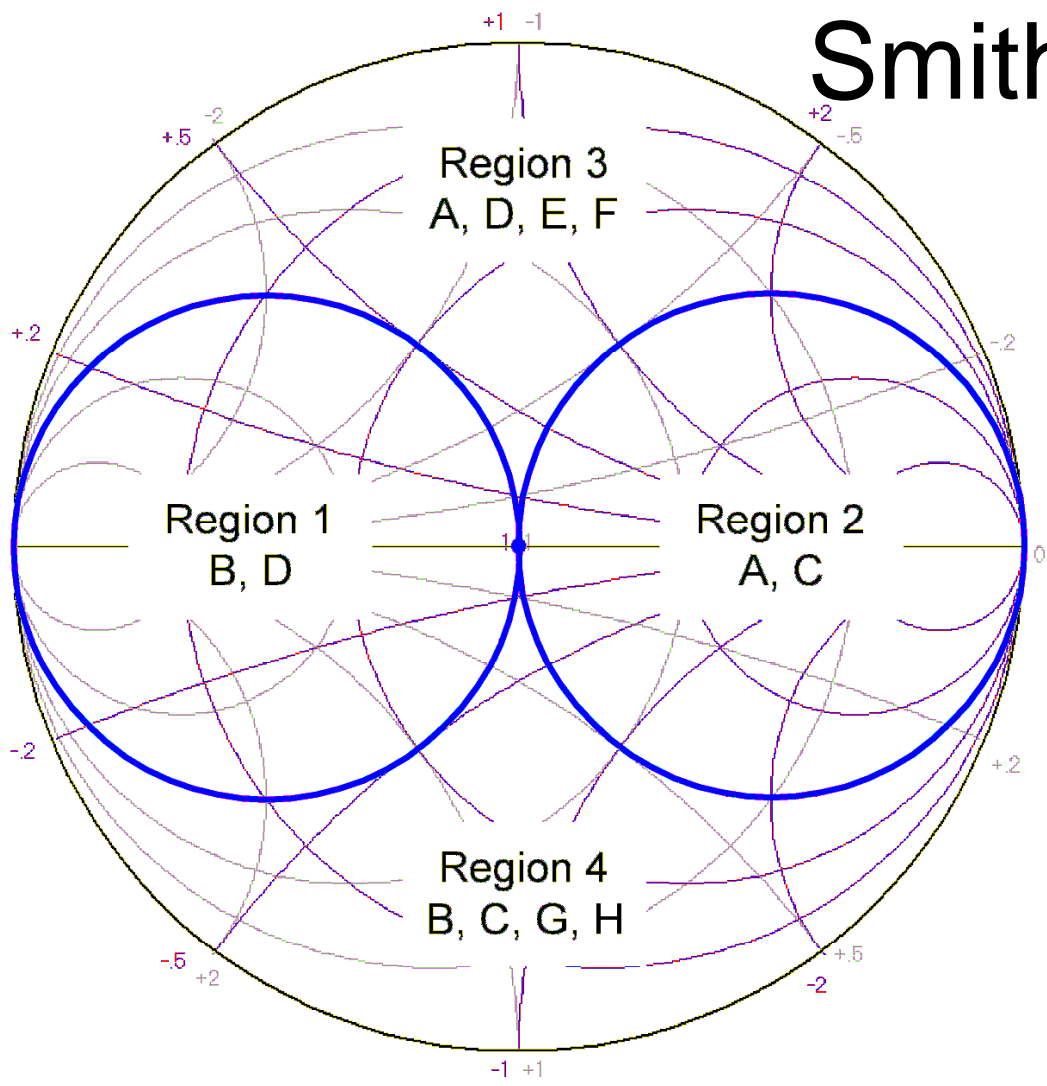

L type circuits

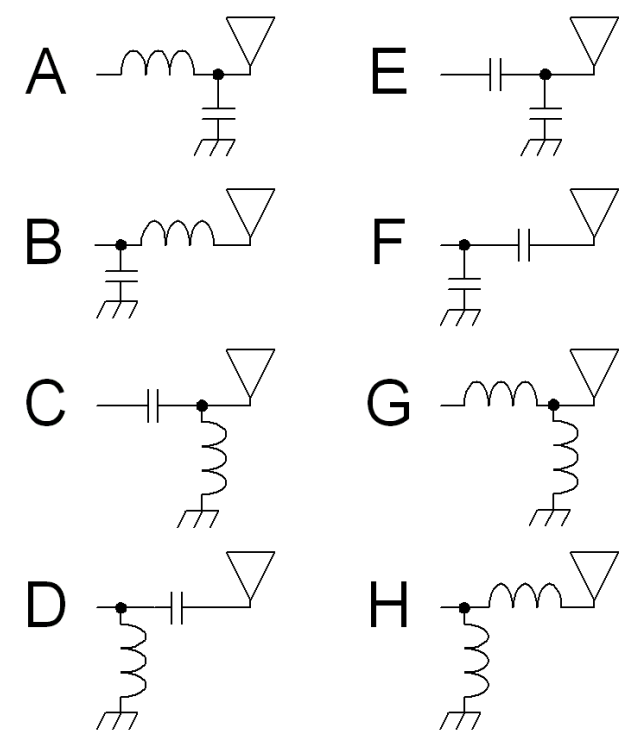

Surge Impedance Again

- $Z_0 = \sqrt{L/C}$ per unit length, equivalent circuit no loss
- $Z_0 = \left(\frac{138}{\sqrt{\epsilon}} \right) * \log_{10} \left(\frac{OD}{ID} \right)$ for round coax
- Why a particular impedance?
 - Maximum power 30Ω, minimum loss 77Ω, max. voltage breakdown 60Ω (1929 Bell Laboratories Study)
 - Maximum power per pound of copper 52Ω (F. Terman?)
 - Today 75Ω, 50Ω, 52Ω, 53.5Ω, 25Ω, 80Ω, 93Ω, etc.